

Q1] $F = (P+Q+R)(\bar{P}+Q)(\bar{Q}+R)$

Taking complement of above expⁿ

$$\bar{F} = (P+Q+R)(\bar{P}+Q)(\bar{Q}+R)$$

Applying De-Morgan's law:

$$\bar{F} = (\overline{P+Q+R}) + (\overline{\bar{P}+Q}) + (\overline{\bar{Q}+R})$$

$$\bar{F} = \bar{P}.\bar{Q}.\bar{R} + P\bar{Q} + Q\bar{R} \longrightarrow \text{option D}$$

$$\bar{F} = \bar{Q}(\bar{P}\bar{R} + P) + Q\bar{R}$$

$$= \bar{Q}[(\bar{P}+P)(P+\bar{R})] + Q\bar{R}$$

$$= \bar{Q}[P+\bar{R}] + Q\bar{R}$$

$$= P\bar{Q} + \bar{Q}\bar{R} + Q\bar{R}$$


$$= P\bar{Q} + (\bar{Q}+Q)\bar{R}$$

$$= P\bar{Q} + \bar{R} \longrightarrow \text{option B}$$

$$= (P+\bar{R})(\bar{Q}+\bar{R}) \longrightarrow \text{option C}$$

Q2] $(\bar{P}+\bar{Q})(R+S)$

ANS = 4

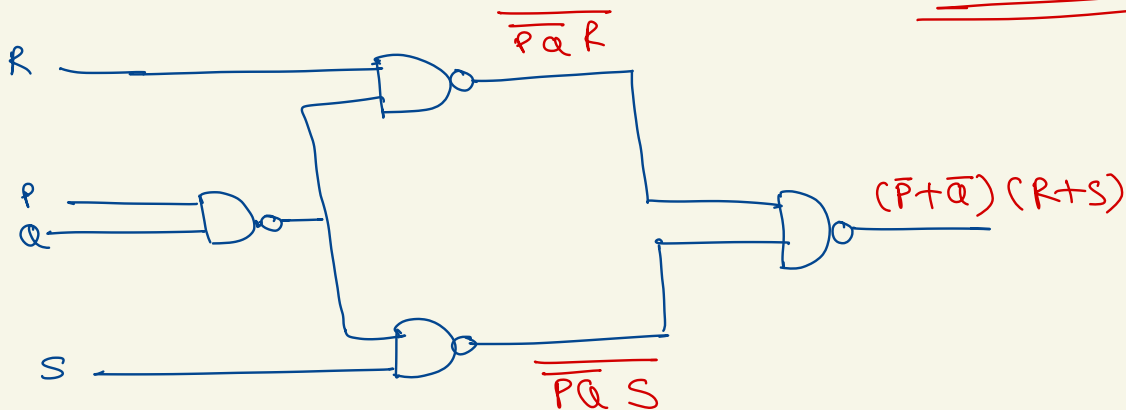

Q3] ✓ A) $\Rightarrow \overline{x \oplus y} = \overline{x \bar{y} + \bar{x} y} = (\overline{x \bar{y}})(\overline{\bar{x} y}) = x y + \bar{x} \bar{y} = x \odot y$

✓ B) $\Rightarrow \bar{x} \oplus y = \bar{x} \bar{y} + x y = x \odot y$

✓ C) $\Rightarrow \bar{x} \oplus \bar{y} = \bar{x} y + x \bar{y} = x \oplus y$

option D

✗ option D

LHS $\Rightarrow (x \oplus \bar{x}) \oplus y$

$$= 1 \oplus y$$

$$= \bar{y}$$

RHS $\Rightarrow (x \odot \bar{y}) \odot \bar{y}$

$$= 0 \odot \bar{y}$$

$$= y$$

Q4]

1. Overflow Condition

- Arithmetic operations have a potential to run into a condition known as *overflow*.
- Overflow occurs with respect to the **size of the data type** that must accommodate the result.
- Overflow indicates that the result was *too large* or *too small* to fit in the original data type.
- When two **signed** 2's complement numbers are added, overflow is detected if:
 - both operands are positive and the result is negative, or
 - both operands are negative and the result is positive.
- When two **unsigned** numbers are added, overflow occurs if
 - there is a **carry out** of the leftmost bit.

option C is correct

$$\begin{array}{r}
 x_7(1) \\
 \underline{y_7(1)} \\
 s_7(0) \\
 \hline
 x_7 y_7 \bar{s}_7
 \end{array}
 +
 \begin{array}{r}
 x_7(0) \\
 \underline{y_7(0)} \\
 s_7(1) \\
 \hline
 \bar{x}_7 \bar{y}_7 s_7
 \end{array}$$

Q5] As per arrangement of MUX, choose BAC, B:MSB, C:LSB

	B	A	C	
x ₀	0	0	0	1 → Due to A', 1 → Due to A'C'
x ₁	0	0	1	1 → Due to A'
x ₂	0	1	0	0
x ₃	0	1	1	1 → Due to AB'C
x ₄	1	0	0	1 → Due to A', 1 → Due to A'C'
x ₅	1	0	1	1 → Due to A'
x ₆	1	1	0	0
x ₇	1	1	1	0

$$x_0 x_1 x_2 x_3 x_4 x_5 x_6 x_7 = 11011100$$

Q6] AB \ CD

	00	01	11	10
00	1		d	1
01		1	1	
11	d			d
10	d	1	1	d

ANS = 3

Q7] KMAP simplification

$$(C' + A)' = CA'$$

we need only 1 NOR gate as all inputs are given