




CS230: Digital Logic Design and Computer Architecture

Lecture 11: Intro. to Single cycle CPU

<https://www.cse.iitb.ac.in/~biswa/courses/CS230/autumn23/main.html>

<https://www.cse.iitb.ac.in/~biswa/>

 Phones
(smart/non-smart)
on silence plz,
Thanks



Single Cycle Processor

- All operations – single cycle 😊
- Clock cycle (unit of time) will be defined based on the longest instruction.
- Two paths of interest: datapath and control. Control tells datapath what to do.
- Do not forget the stored program concept.

Clock Cycle

Tick, clock tick, clock period, clock, clock cycle, or cycle

Discrete time intervals

Based on processor frequency (clock rate)

1GHz processor, clock cycle = 1ns


4GHz processor, clock cycle = 0.25ns



Let's start with the datapath

Anything that stores data or operates
on data, within a processor


Instruction Memory

 

Remember: No writes to instruction memory 😊


Not concerned about how programs are loaded into this memory.

Program Counter

 


Remember: No writes to instruction memory 😊


Register File

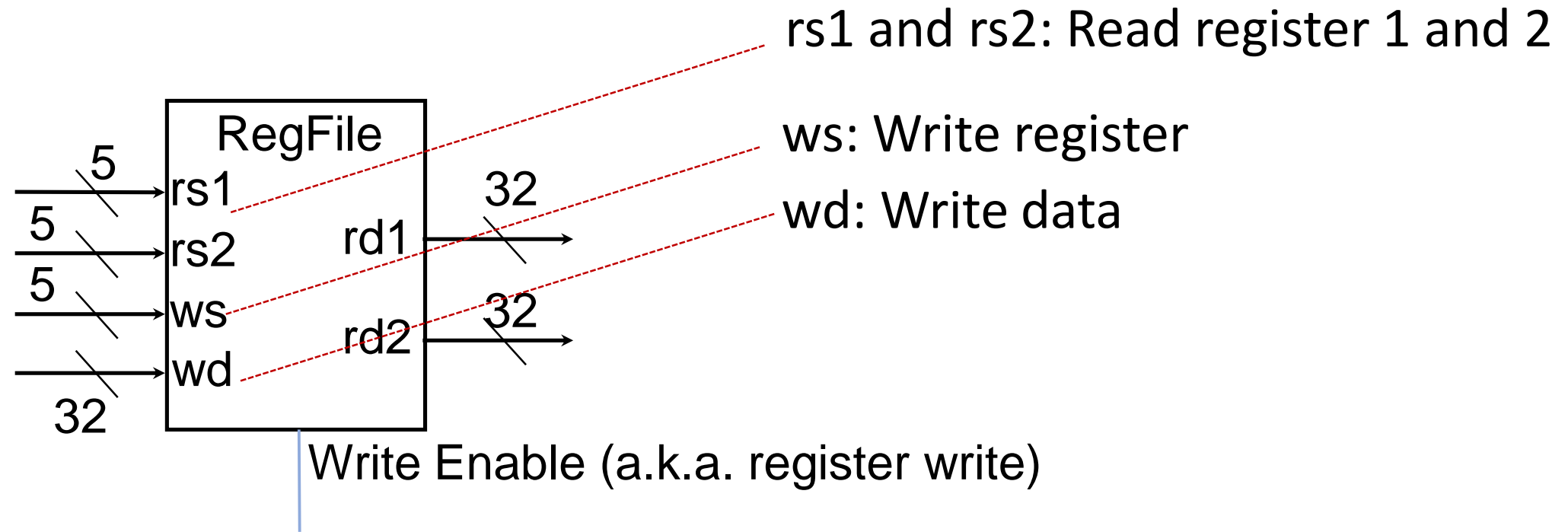

The ALU

 


Data Memory

 

Why data and instruction
memory and not one memory?
Later in the course 😊


Address and Data Bus (Instruction Fetch)

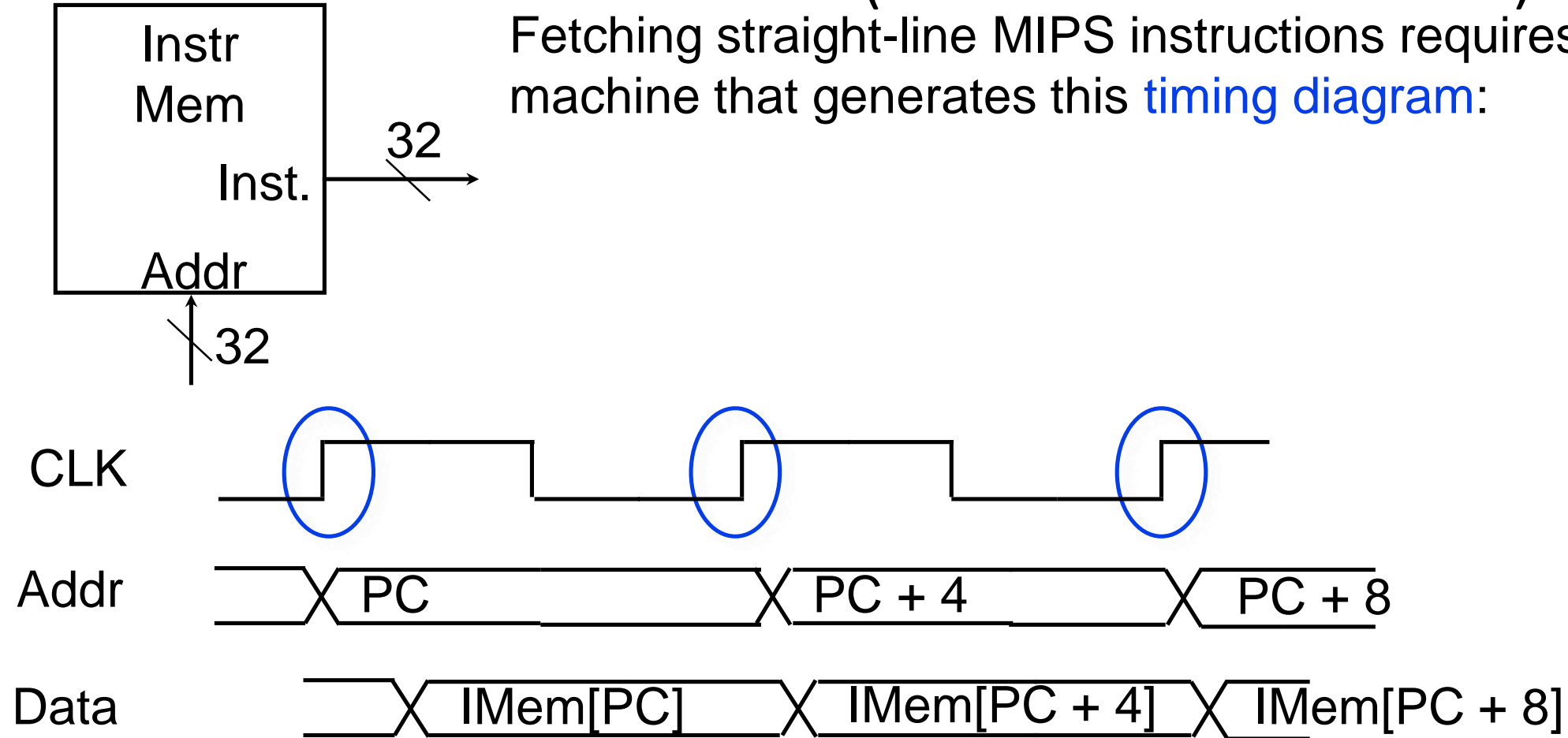Fetching straight-line MIPS instructions requires a machine that generates this [timing diagram](#):




PC == Program Counter, points to next instruction.

Decode and Execute

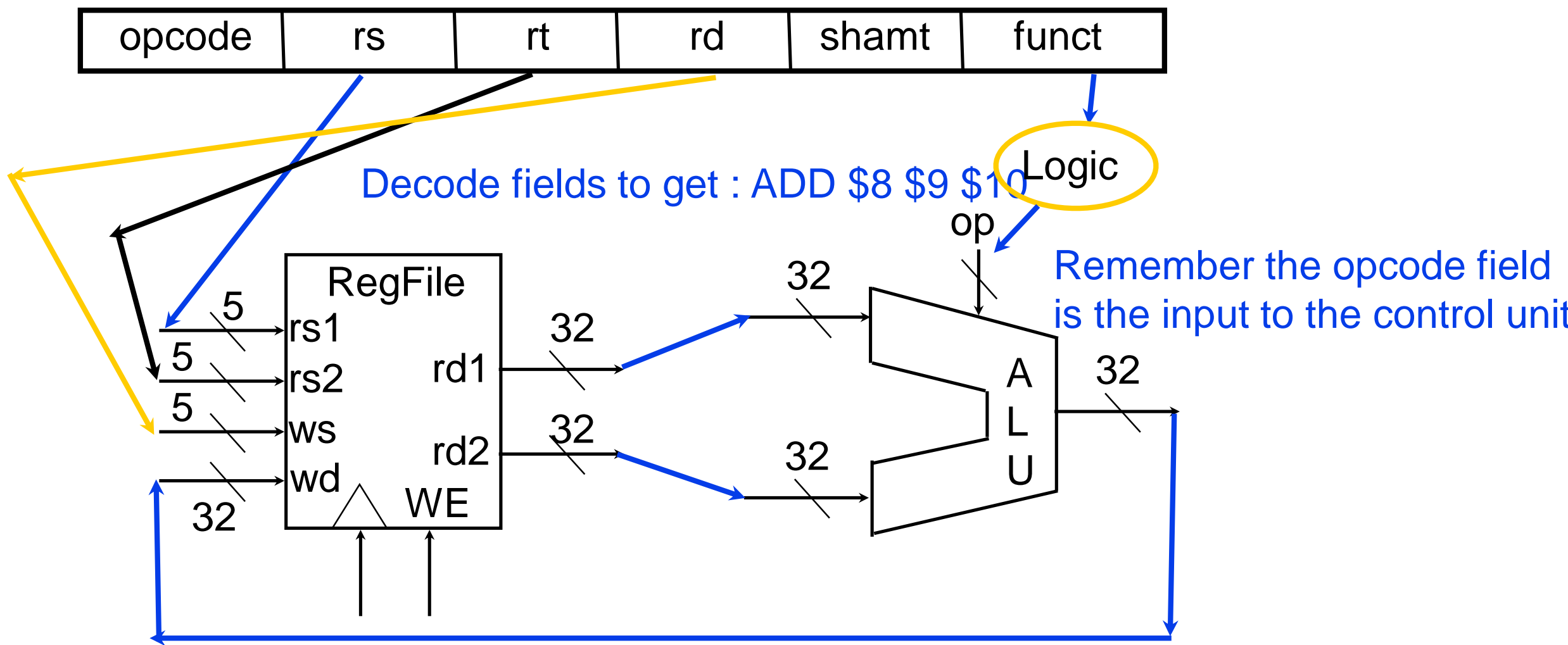


All in one go

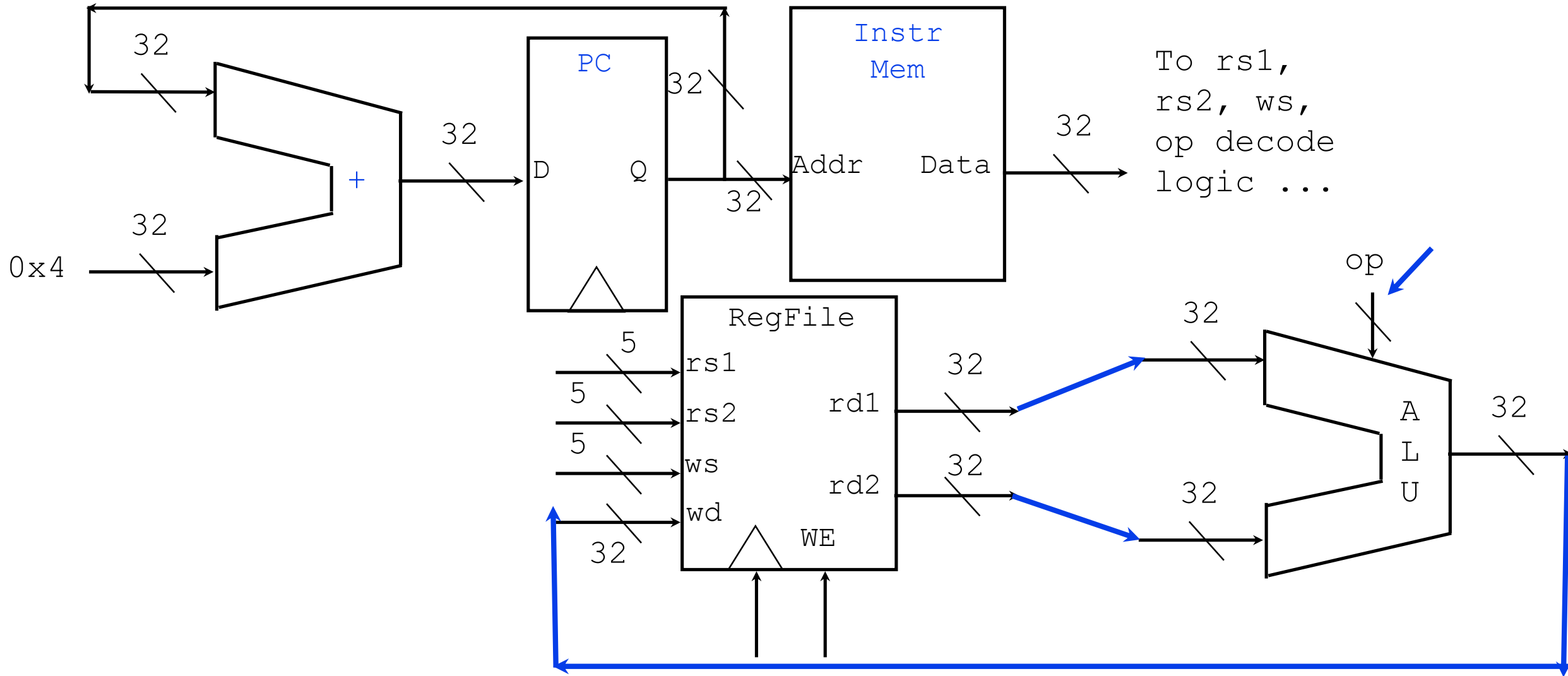


To rs1,
rs2, ws,
op decode
logic ...

What about I format?

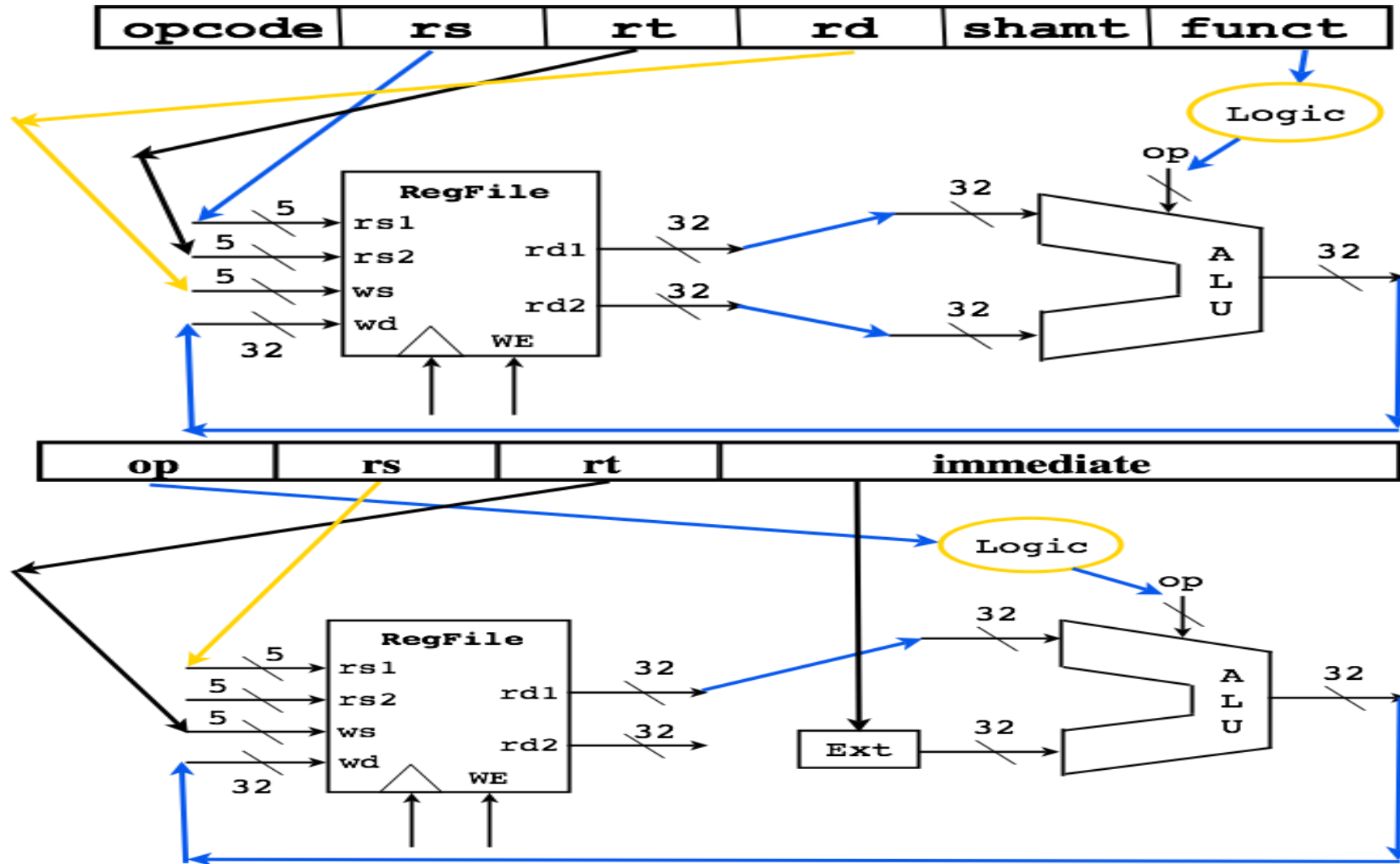

Loads from Memory

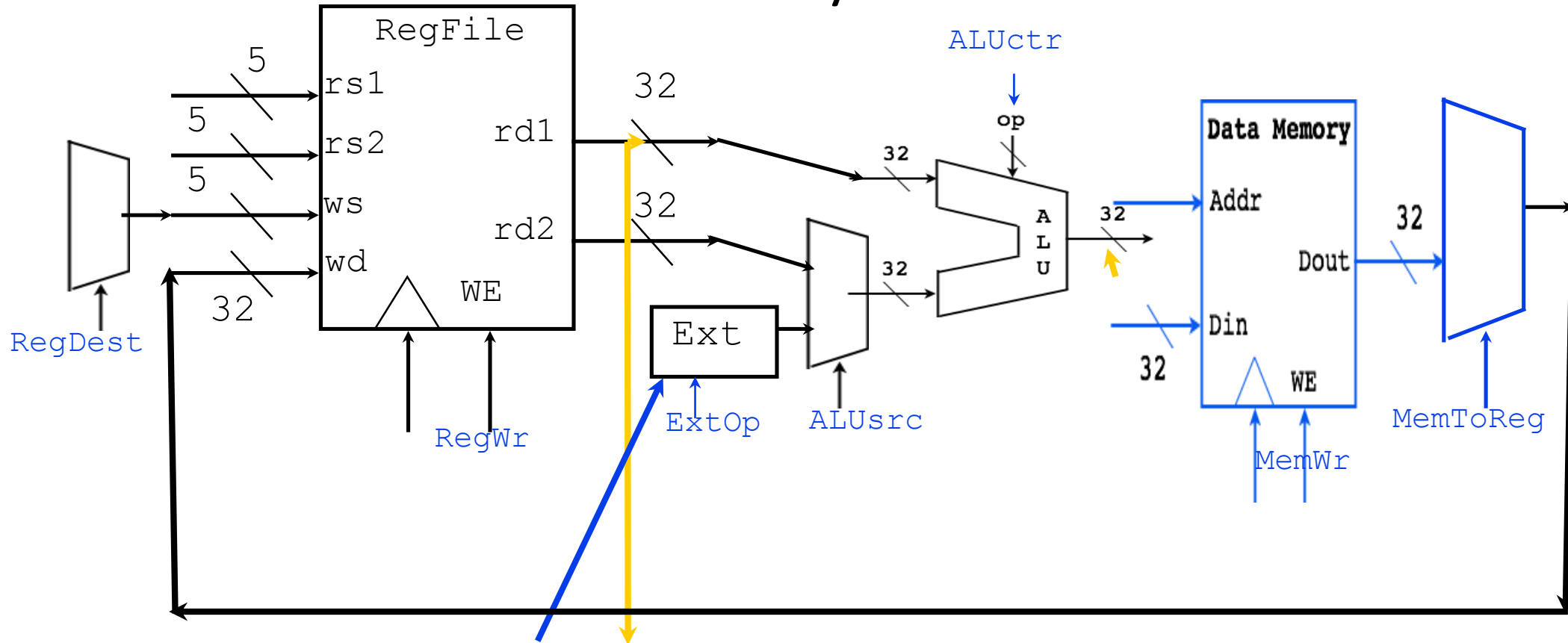

Syntax: LW \$1, 32(\$2)


Action: $\$1 = M[\$2 + 32]$

Branch Instructions

Syntax: BEQ \$1, \$2, 12


Action: If (\$1 != \$2), PC = PC + 4

 Action: If (\$1 == \$2), PC = PC + 4 + 48



Control Signals So far

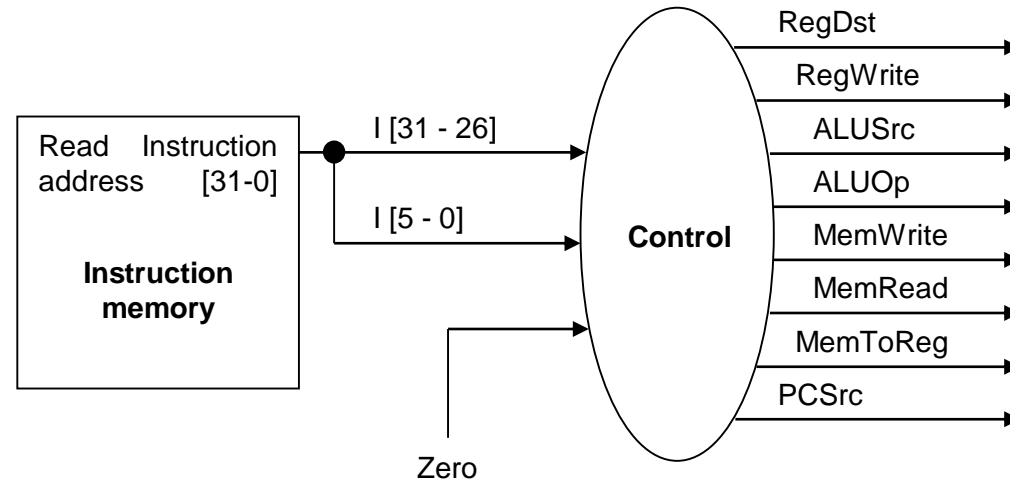- MemRead
- MemWrite
- RegWrite
- MemtoReg
- RegDst
- ALUOp, ALUSrc
- PCSrc (we have not discussed about the branch)




In detail

- MemRead: Read from memory when **assert**
- MemWrite: Write into the memory when **assert**
- RegWrite: Reg. on **Write register** updated with the input, **on assert**
- MemtoReg: On **assert**, memory to register, on **deassert**, ALU to register
- RegDst: On **assert**, use rd field, on **deassert** use rt field
- ALUSrc: On **assert**, lower 16 bits of an inst., on **deassert** from the second register
- PCSrc: On **assert**, branch target, **deassert**, PC+4

Control Signal Table

Operation	RegDst	RegWrite	ALUSrc	ALUOp	MemWrite	MemRead	MemToReg
add	1	1	0	010	0	0	0
sub	1	1	0	110	0	0	0
and	1	1	0	000	0	0	0
or	1	1	0	001	0	0	0
slt	1	1	0	111	0	0	0
lw	0	1	1	010	0	1	1
sw	X	0	1	010	1	0	X
beq	X	0	0	110	0	0	X

The Complete Picture

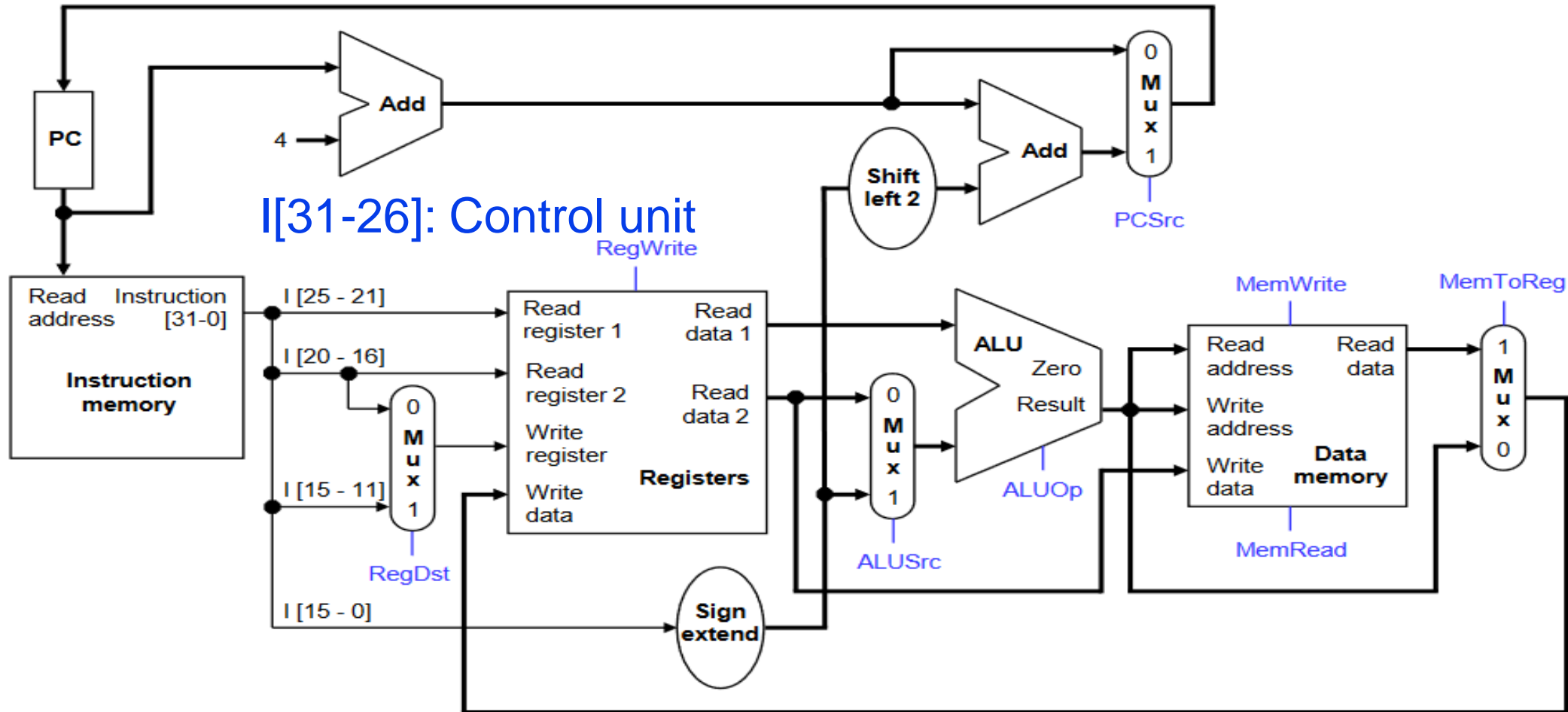

Why not single cycle?

- The longest possible datapath is the clock cycle time.

What does it mean?

Why not single cycle?


- For example, `lw $t0, -4($sp)` needs 8ns, assuming the delays shown here.

reading the instruction memory	2ns	} 8ns
reading the base register \$sp	1ns	
computing memory address \$sp-4	2ns	
reading the data memory	2ns	
storing data back to \$t0	1ns	

one clock cycle: 8ns

Processor frequency: 125MHz

Cycle per Instruction (CPI): 1

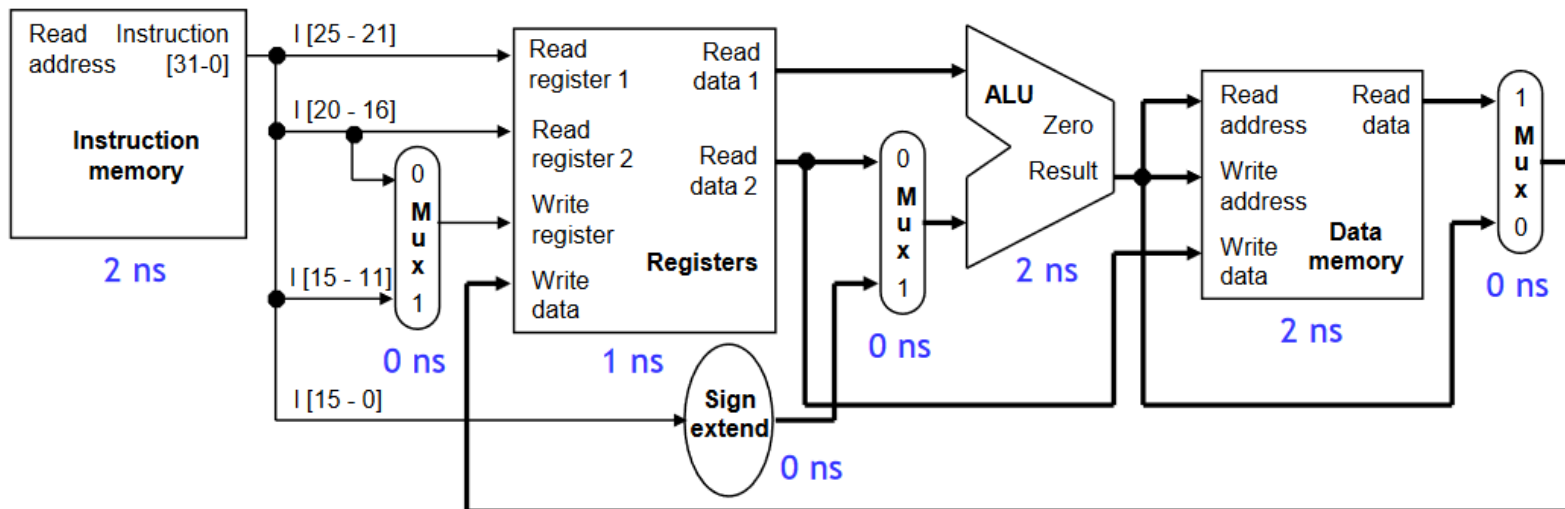


An add instruction:
no need of 8ns

Why not single cycle?

- The longest possible datapath is the clock cycle time.

Violating *common case fast (Confucius says)*

Oh No! Such a bad design

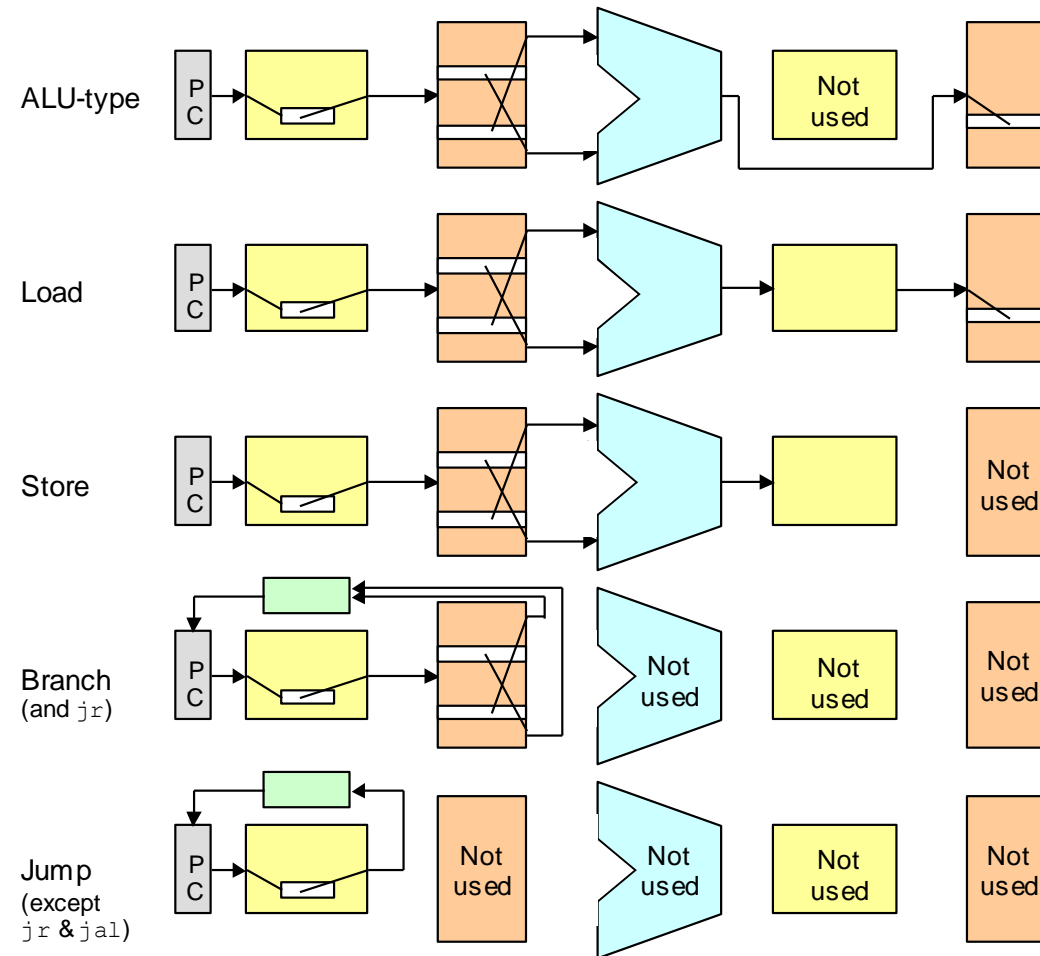

Single to Multi Cycle

