

CS305


Computer Architecture

Bus Interfacing

Bhaskaran Raman
Room 406, KR Building
Department of CSE, IIT Bombay


<http://www.cse.iitb.ac.in/~br>

Bus Interfacing

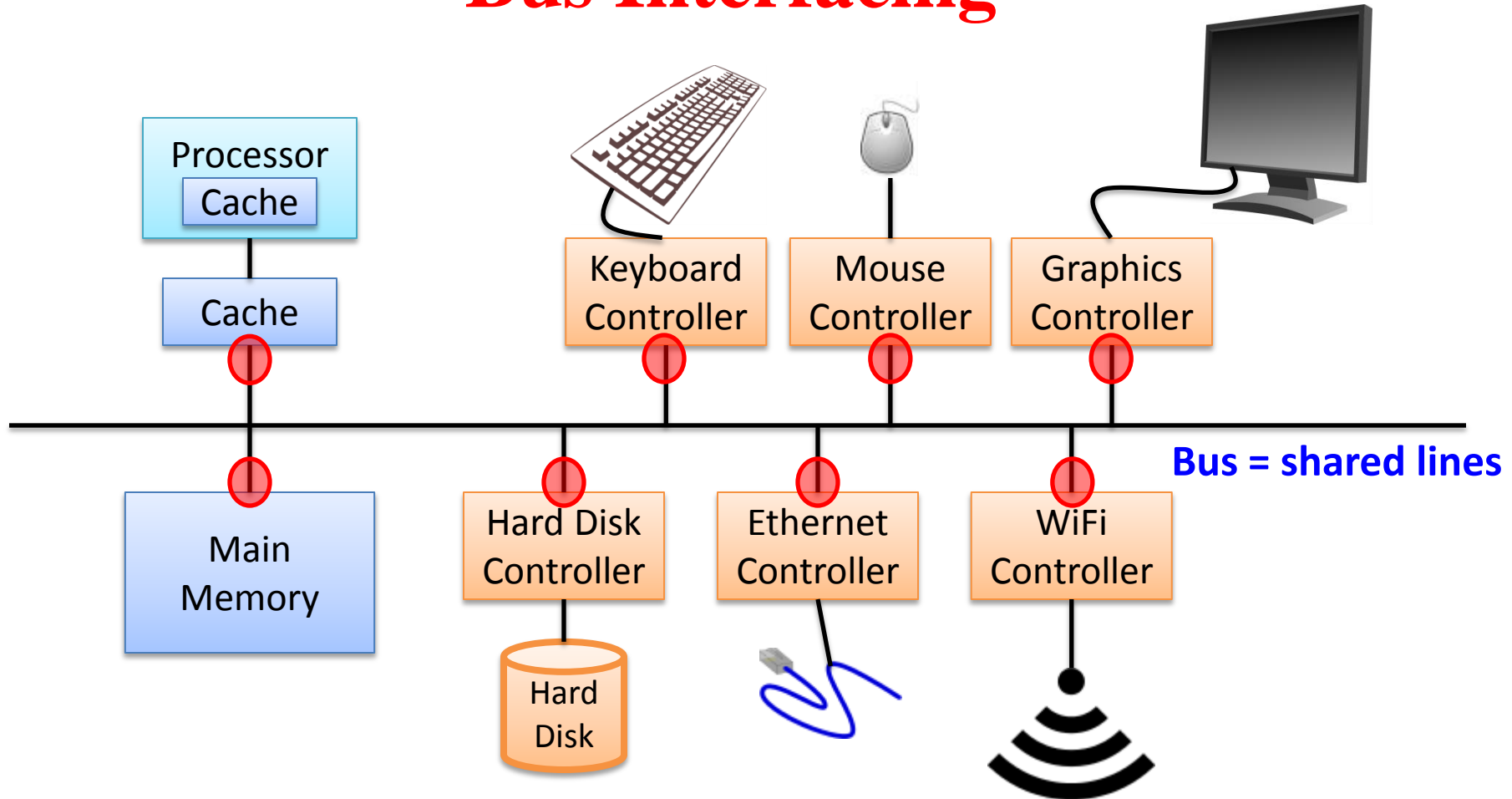


Bus Interfacing: Tri-Stating

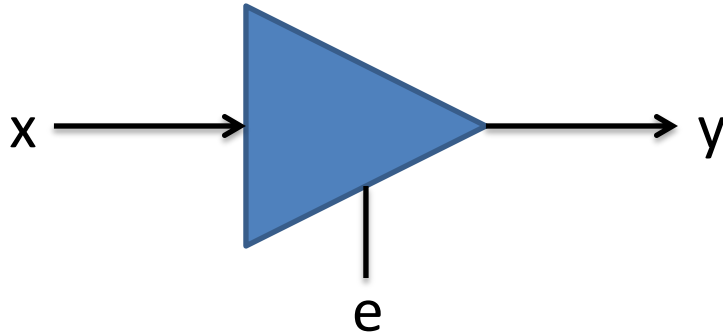Bus interface can be in 1 of 3 states:
0 (low voltage), 1 (high voltage), Z (disconnected, high impedance)



If ($e==1$), $y=x$
Else, $y=Z$ (disconnected from x)

How Tri-Statting Works

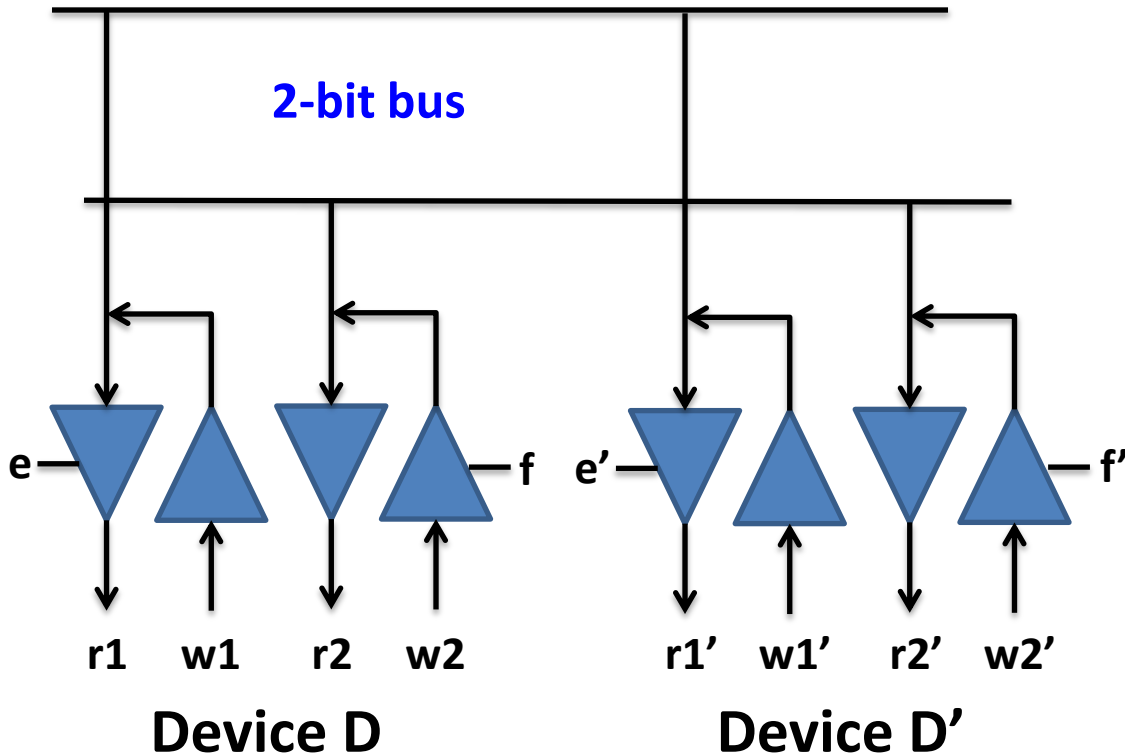

- D is writing to D'
 - $e=0, f=1, e'=1, f'=0$
- D' is writing to D
 - $e=1, f=0, e'=0, f'=1$
- $e=f=0 \rightarrow$ D is tri-stated
 - D is disconnected from bus
- $f=f'=1 \rightarrow$ bus protocol error

Advantages of Tri-Stating

- Bus fan-out can be high
 - Most devices tri-stated most of the time anyway!
- Same bus-line can be used for input and output
 - Note: not all devices may need to drive (write to) all bus lines
 - E.g. memory need not drive address lines