

CS230: Digital Logic Design and Computer Architecture

Tutorial 04 [Mon 09 Sep, Tue 10 Sep]

Concepts tested: Single Cycle Implementation, Extension

1. Draw the hardware diagram for the single cycle implementation of the MIPS instruction subset **add**, **sub**, **and**, **or**, **slt**, **lw**, **sw**, **beq**.
2. Identify the control lines in the above implementation and draw the truth table for the (main) control unit.
3. Extend the above datapath to support **{lb, lbu}**; that is, the signed and unsigned versions of the load-byte instruction. Show *only the changes* to the original datapath.
4. Show the modified truth table to generate the controls; mention just the changes/additions from the earlier table.
5. Extend the original datapath to support a new instruction **ldpc**, which loads the value of **PC+4** onto a given register (no need to include support for **lb**, **lbu** here).
6. Show the modified truth table to generate the controls; mention just the changes/additions from the earlier table.