

CS305

Computer Architecture

Multi Cycle Implementation of MIPS ISA (Subset)

Bhaskaran Raman
Room 406, KR Building
Department of CSE, IIT Bombay

<http://www.cse.iitb.ac.in/~br>

Multi-Cycle Implementation: Overall Idea

- High level fixes from single-cycle implementation:
 - Reuse hardware components
 - Each instruction executes only as long as necessary
- Main changes to incorporate these fixes:
 - I and D memory the same
 - $PC+4$, BrTgt also computed using main ALU
 - Latches between main hardware components: remember values across cycles
 - Control will become much more complex!


MIPS ISA Subset

- Reg-reg: **add**, **sub**, **and**, **or**, **slt**
- Memory: **lw**, **sw**
- Branch: **beq** (and **j** later)
- Subset → keep it simple, understand techniques


The Three Modules in Multi-Cycle Implementation

- I+D memory
- Register File
- ALU


Data-Path, Control Changes: I+D Mem

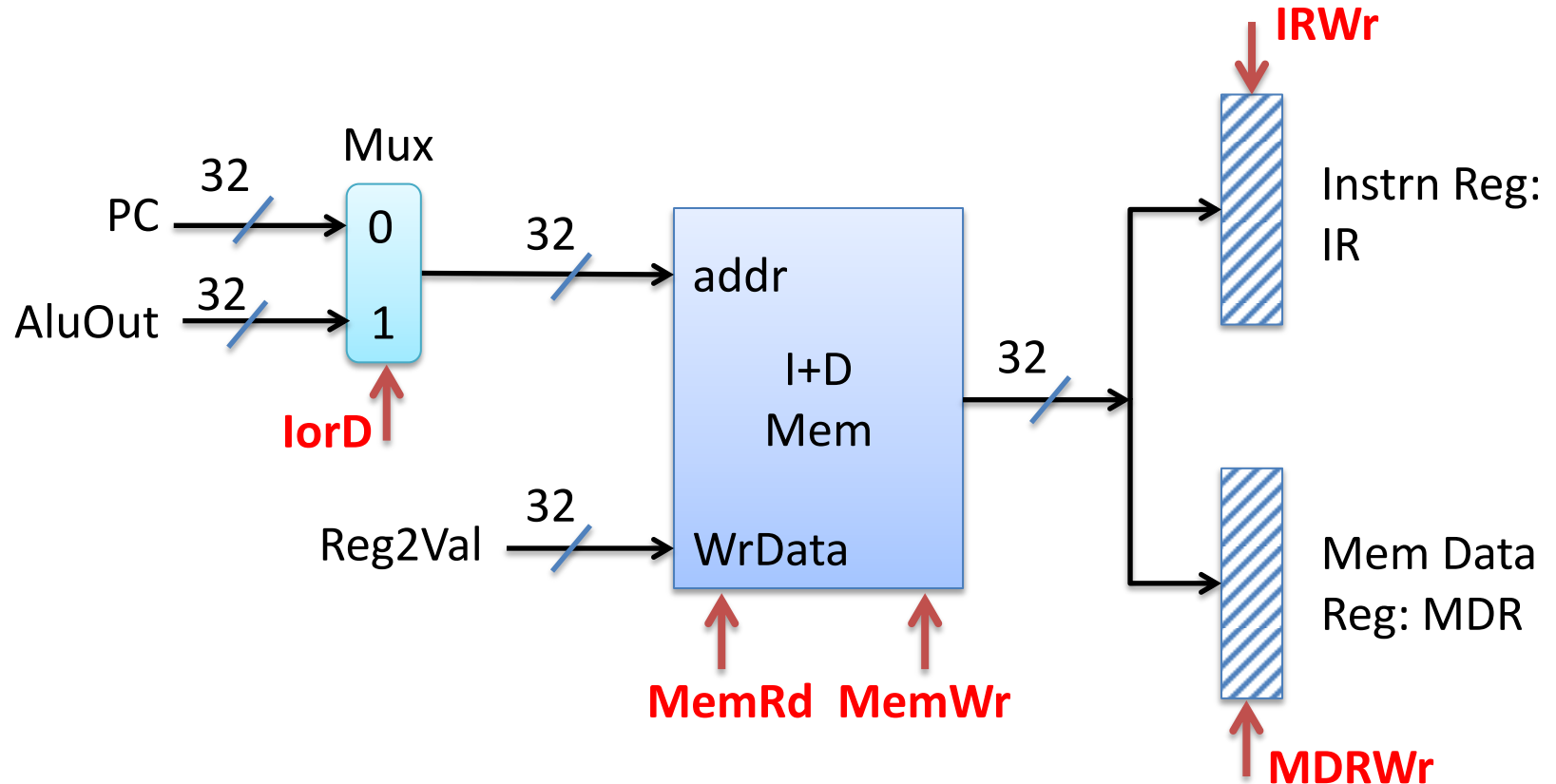

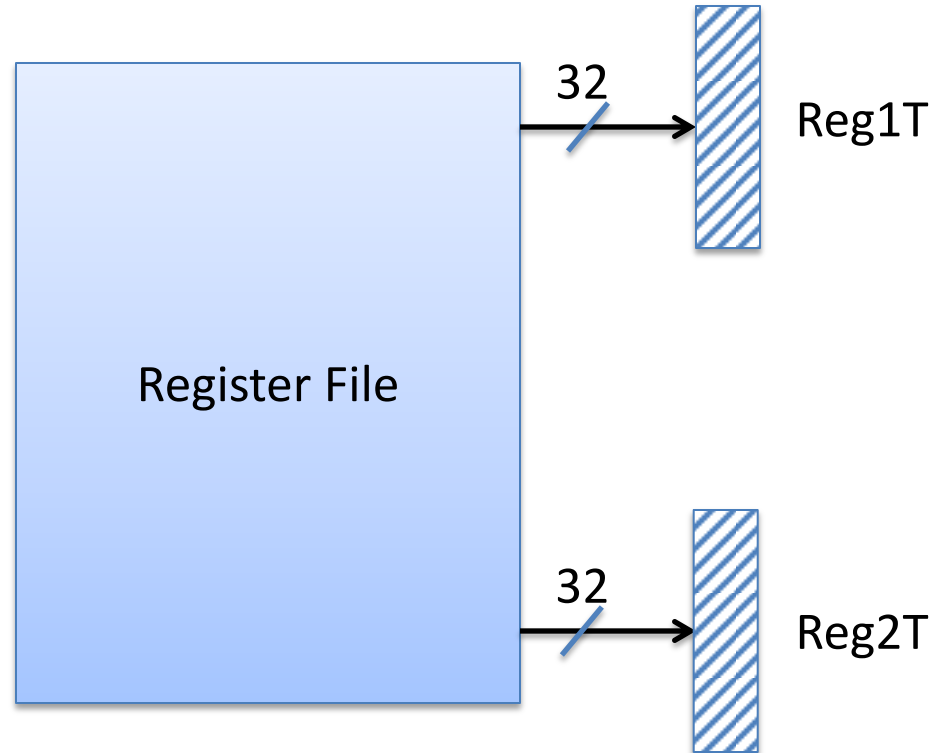
Data-Path, Control Changes: Register File



Data-Path, Control Changes: ALU

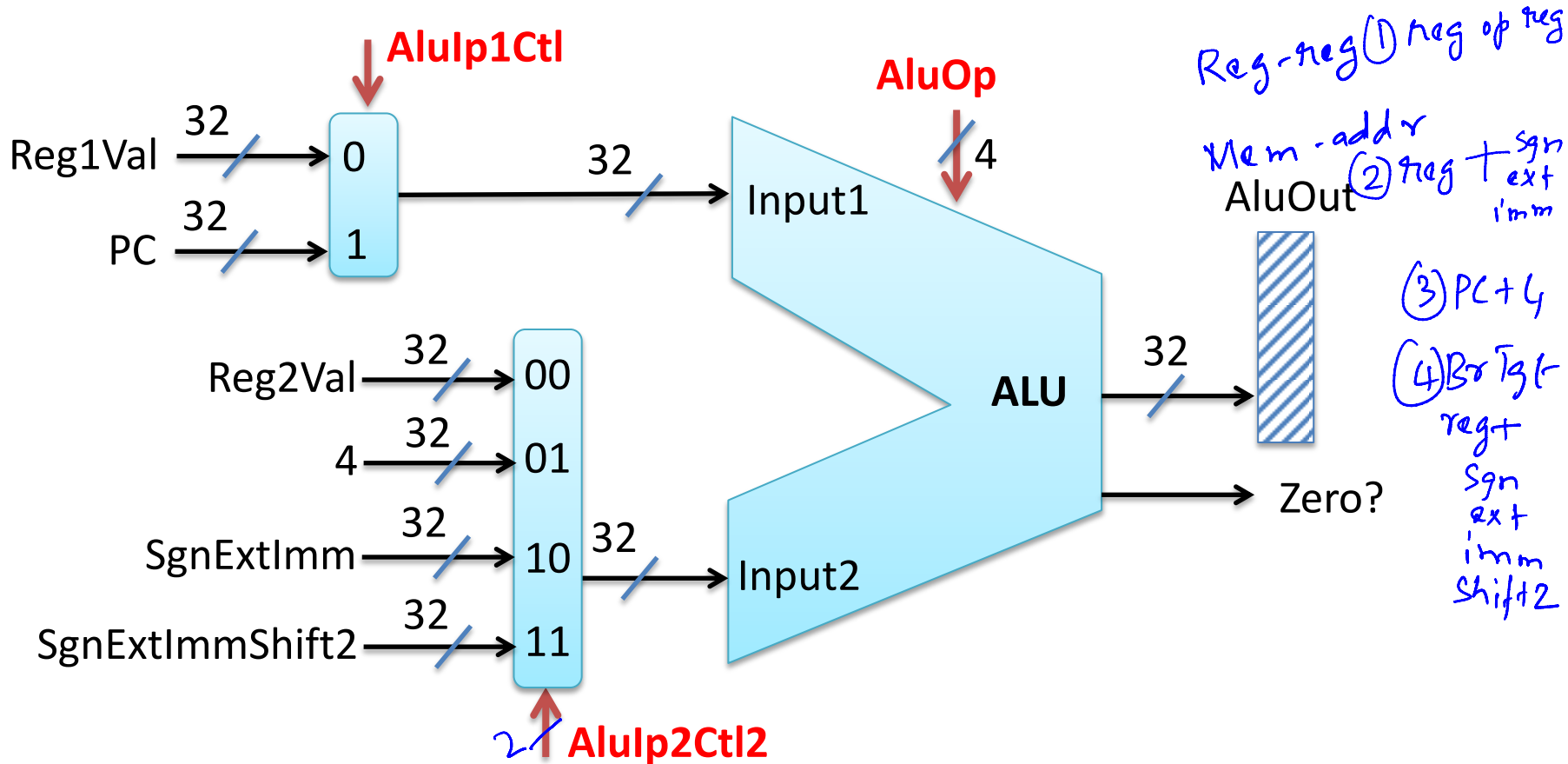

Data-Path, Control Path Changes: PC

 

Summary of Data Path Changes

- 3 modules: I+D mem, RegFile, ALU
- Changes to input of each: for reuse
 - Control lines to select input
- Output of each: to latch, to carry result to next cycle
 - Control lines to enable write

The Execution Plan: Definition

- Multi-cycle also called multiple *stages*
- Execution Plan: what happens in each *stage/cycle* of an instruction
 - In terms of how each module is used, for what purpose

The Execution Plan

Stage-1:

- (a) Instruction fetch
 $IR = Mem[PC]$
- (b) $PC = PC + 4$

Stage-2:

- (a) Register read
 $Reg1T = Reg[Rs]$
 $Reg2T = Reg[Rt]$
- (b) Compute BrTgt
 $ALUOut =$
 $(PC + 4) + SgnExtImmShift2$

Stage-3: reg-reg

- (a) ALU operation
 $ALUOut = Reg1T \text{ op } Reg2T$

Stage-3: lw, sw

- (a) Mem addr computation
 $ALUOut = Reg1T + SgnExtImm$

Stage-3: beq

- (a) Branch condition check
 $ALUOut = Reg1T - Reg2T$
 $zero? = (ALUOut \neq 0)$
- (b) If zero?, $PC = BrTgt (ALUOut)$

The Execution Plan (Continued)

Stage-4: reg-reg

(a) Write back ALUOut to RegFile

Stage-4: lw

(a) Read memory
 $\text{MDR} = \text{Mem}[\text{ALUOut}]$


Stage-4: sw

(a) Write memory
 $\text{Mem}[\text{ALUOut}] = \text{Reg2T}$

Stage-5: lw

(a) Write back to RegFile from
MDR

Overwriting PC: The Two Options

 

Summary

- Changes to multi-cycle implementation
 - Input muxes, Latches, Control lines
- Execution plan
 - Stage-by-stage description of instruction execution
- Next: logic for generation of control lines