
CS230: Practice Problem Set 1 (Autumn 2024)

Date posted: August 13, 2024

These are ungraded practice questions. You are strongly encouraged to solve these independently to ensure you understand the content taught in class.

- Given $X = 0001001111110000$ and $Y = 0000110001011111$. Calculate $Z = X - Y$ using 2's complement subtraction.
 - For example, $Z = 0000110011001100$, the positions of set bits (LSB is position 0) in Z will be the minterms. So, in this case $Z = \sum m(2, 3, 6, 7, 10, 11)$. Minimize the computed Z from (a) using a K-map.
- Implement the below expression using a single 8 x 1 MUX.
 $F(A, B, C, D) = \sum m(1, 3, 4, 11, 12, 13, 14, 15)$.
- By now, you must have figured out that NAND and NOR gates are universal gates (any Boolean logic circuit can be constructed using only NAND gates or NOR gates). Find out the minimum number of 2-input NAND gates or NOR gates (find both the counts) required to implement:
 - Half Adder
 - Full Adder
 - Full Subtractor
- Let m and n be the number of input lines and output lines, respectively, for a decoder that is used to uniquely address a byte-addressable 1 GB RAM, then what is the minimum value of $m+n$?
- Design a four-input priority encoder with the help of the table given below. D0 has the **highest** priority, and D3 has the **lowest** priority.

Inputs				Outputs		
D3	D2	D1	D0	A	B	C
0	0	0	0	X	X	0
X	X	X	1	0	0	1
X	X	1	0	0	1	1
X	1	0	0	1	0	1
1	0	0	0	1	1	1

Table 1: Truth Table for Priority Encoder

- How many 3-to-8 line decoders with an enable input are needed to construct a 6-to-64 line decoder without using any other logic gates?

7. Assume a full adder has a worst-case delay of 15 ns for *sum* output and 12 ns for *carry* output. If such adders are used to design a 16-bit ripple carry adder, then compute the worst-case delay of the circuit.
8. If instead of a ripple carry adder design for a 16-bit adder, we use a cascade of four 4-bit carry-lookahead adders, each of which has a worst-case delay of 25 ns for its *carry* output and worst-case delay of 30 ns for its *sum* outputs, then find the worst-case delay of such a 16-bit adder.
9. Let $f(w, x, y, z) = (w'x'y'z' + w'x'y'z + w'xyz' + w'xyz + wx'y'z' + wx'yz)$ be the given function of 4 variables w, x, y, z .
Suppose only a single 4 x 1 MUX and a single 2-input XOR gate is available. Although inverters are available in plenty. Implement the above logic function using signals w, x to drive the select inputs s_1, s_0 of the multiplexer and single XOR gate and a **minimum** number of inverters.
Express your solution uniquely by describing the logic expressions for the 4 data inputs d_0, d_1, d_2, d_3 of the multiplexer. Note that these expressions should adhere to the restriction of using a **single XOR** gate and a **minimum number of inverters**.
10. Using a 4 x 1 MUX with select inputs S_1, S_0 as A, B , implement the following function: $F(A, B, C, D) = \sum m(3, 4, 6, 9, 10, 11, 13, 14)$.
Draw the circuit. Assume complements of inputs are available. In addition, you may use NOT, OR, AND or XOR gates. An **inefficient** implementation (unnecessary use of gates) will **not** receive full credits.
11. What is the value of xyz if the following expression is solved?
 $(11)_2 + (22)_3 + (33)_4 + (44)_5 = (xyz)_6$. a_b denotes a represented with base b .
12. You have to design a two-bit less than comparator logic circuit ($A < B$). The following incomplete circuit is provided to you. Name the appropriate logic gate for each box to complete the circuit.

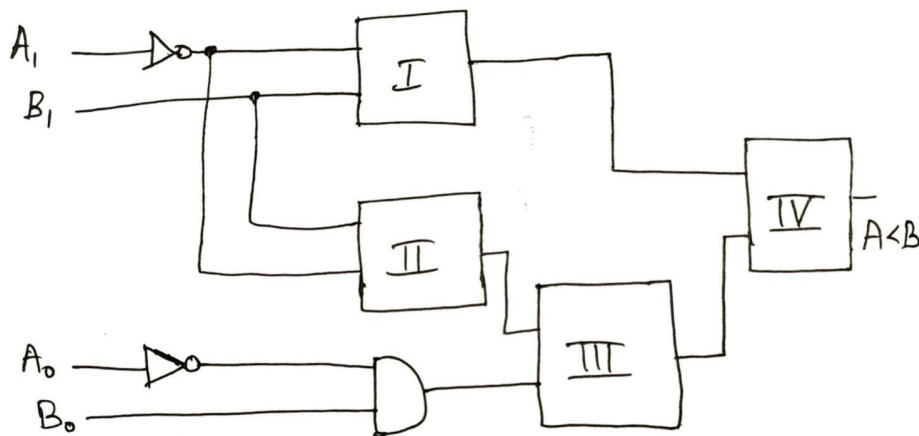


Figure 1: Incomplete circuit for Q.12

13. Minimize and realise the function $f = \overline{\overline{\overline{A + [B + \overline{C} \cdot (\overline{A \cdot B + A \cdot \overline{C}})]}}}$ using minimum number of 2-input NOR gates.
 14. Find dual and complement of the function $F = \overline{X \cdot Y \cdot Z + \overline{X} \cdot \overline{Y}} + Y \cdot Z$
 15. What is the minimum number of 2-input NOR gates required to implement a 4-variable function represented in the form of minterms as, $f = \sum m(0, 2, 5, 7, 8, 10, 13, 15)$? Draw the circuit.
 16. Give the map of an irreducible four-variable function whose sum-of-products represents 2^3 minterms. Prove that there exists a function of n variables whose minimal sum-of-products form consists of 2^{n-1} minterms and that no function, when expressed in sum-of-products form, requires more than 2^{n-1} product terms. Derive a bound on the number of literals needed to express any n -variable function.
 17. For the three functions shown below, obtain a multi-output minimized two-level implementation using an augmented prime implicant chart. Assume that minimizing the total number of gates is the sole objective.
 - (a) $f1 = \sum(2, 3)$
 - (b) $f2 = \sum(2, 3, 4, 5, 6, 7)$
 - (c) $f3 = \sum(1, 3, 5, 7)$
-

Best wishes!

CS230: Practice Problem Set 2 (Autumn 2024)

Date posted: August 14, 2024

These are ungraded practice questions. You are strongly encouraged to solve these independently to ensure you understand the content taught in class.

1. Consider a sequential digital circuit consisting of T flip-flops and D flip-flops as shown in the figure. CLKIN is the clock input to the circuit. At the beginning, Q_1 , Q_2 , and Q_3 have values 0, 1, and 1, respectively.

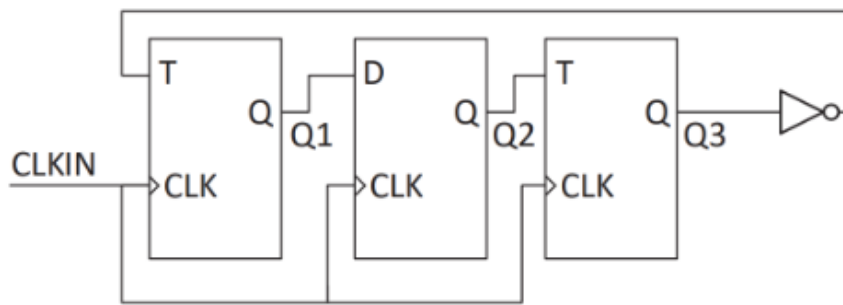


Figure 1: Sequential circuit for Q.18

Analyze the circuit and determine the possible sequences of states for Q_1 , Q_2 , and Q_3 . Determine the sequence of state of Q_1 , Q_2 , and Q_3 that can never occur.

2. Consider the circuit given below with initial state $Q_0 = 1$, $Q_1 = Q_2 = 0$. The state of the circuit is given by the value $4Q_2 + 2Q_1 + Q_0$. Note that this represents the decimal value corresponding to a state. For example, $Q_2 = 1$, $Q_1 = Q_0 = 0$ represents decimal value 4. Find the correct state sequence of the circuit.

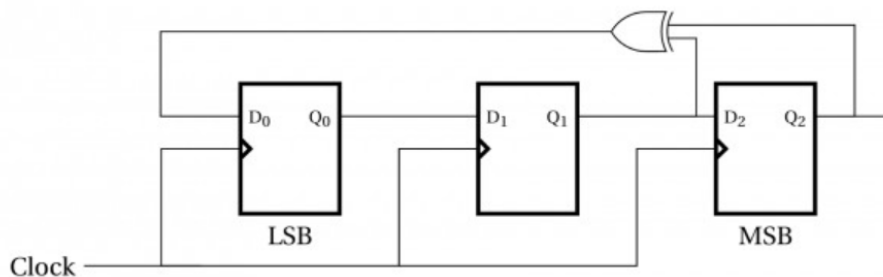


Figure 2: Sequential circuit for Q.2

3. Design a Mealy state machine that detects a sequence '110' in a stream of input bits. The machine should output '1' on the clock cycle following the detection of the sequence and '0' otherwise. Your design should minimize the number of states and transitions.
 - (a) Draw the state diagram.
 - (b) Derive the state transition table.
 - (c) Implement the circuit using D flip-flops and logic gates.
4. A sequential circuit with two D flip-flops A and B , two inputs x and y , and one output z is specified by the following next-state and output equations:

$$A(t+1) = x'y + xB$$

$$B(t+1) = x'A + xB$$

$$z = A$$
 - (a) Draw the logic diagram of the circuit.
 - (b) List the state table for the sequential circuit.
 - (c) Draw the corresponding state diagram.
5. Design a sequential circuit with two JK flip-flops A and B and two inputs E and F . The circuit should operate according to the following rules:
 - (a) If $E = 0$, the circuit remains in the same state regardless of the value of F .
 - (b) When $E = 1$ and $F = 1$, the circuit should go through the state transitions $00 \rightarrow 01 \rightarrow 10 \rightarrow 11 \rightarrow 00$ and repeat.
 - (c) When $E = 1$ and $F = 0$, the circuit should go through the state transitions $00 \rightarrow 11 \rightarrow 10 \rightarrow 01 \rightarrow 00$ and repeat.
6. A Door opens if it ever sees the password 101 in a transmission. More formally, this FSM takes a bitstring consisting of 0's and 1's as its input and continually outputs 0's until it sees the substring 101, after which it outputs 1's continuously. Example execution of the FSM Input: 0001000101000101 Output:0000000001111111.

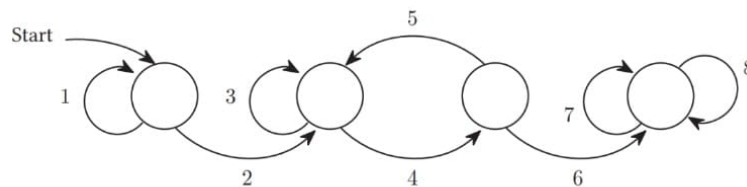


Figure 3: FSM for Q.6

- (a) Mark all the arrows numbered from 1 to 8 with appropriate transitions.

- (b) Modify the above FSM to open the door when it detects the string "0110" in the transition.
 - (c) Extend your FSM to recognize two different patterns: "100" and "010". the FSM should output a continuous 1's after detecting either pattern.
7. Design a sequence detector that identifies the pattern 1101 in any given input, such as 011010110100011 and also detects the pattern 1010. The detector should output a high signal (1) for one clock cycle when either of the sequences is detected. The detector should be able to detect overlapping sequences and sequences that start in the middle of the input stream.
- (a) Draw a state diagram for the sequence detector that detects both patterns 1101 and 1010.
 - (b) Decide whether your designed FSM should be a Mealy and/or Moore machine and provide justification for your design choice.
 - (c) Draw the state diagram of your chosen machine (Mealy/Moore).
 - (d) Draw the state table for your sequence detector. (also check for input stream '0110101101000110001010101101')
8. Design a synchronous counter that counts from 0 to 255 and then wraps around to 0, using only 8 flip-flops and a minimal number of gates.
- (a) Use only 8 flip-flops (D-type or T-type)
 - (b) Use a minimal number of gates (AND, OR, NOT, etc.)
 - (c) The counter should be synchronous, meaning that all flip-flops are clocked simultaneously
 - (d) The counter should count from 0 to 255 and then wrap around to 0
 - (e) The counter should have a single clock input and a single reset input

Hint: You may need to combine binary and gray code to achieve the desired count sequence.

9. Consider the following finite state machine (FSM) table with six states. Minimize the number of states in the FSM using state equivalence while preserving the machine's original behaviour.

Table 1: Table for Q.9

Current State	Input	Next State	Output
A	0	B	0
A	1	C	1
B	0	A	0
B	1	D	1
C	0	E	0
C	1	F	1
D	0	B	0
D	1	C	1
E	0	A	0
E	1	D	1
F	0	C	0
F	1	E	1

- (a) The minimized FSM should have the same input alphabet and output alphabet as the original FSM.
- (b) The minimized FSM should produce the same output sequence for any given input sequence as the original FSM

Hint: You may need to use the concept of state equivalence

Best wishes!

CS230: Digital Logic Design and Computer Architecture

Tutorial 01 [Mon 19 Aug, Tue 20 Aug, Thu 22 Aug]

Concepts tested: Introduction to Computer Architecture, Instruction Set Architecture

1. What is a combinational circuit? What is a combinatorial circuit? What is a sequential circuit?
2. Name a C compiler you have used. In this case, which program was the assembler?
3. The language hierarchy needs some enhancement in the case of Java. Draw the enhanced language hierarchy.
4. Name an obsolete storage device.
5. What is the input device for the “Cell Phone Motor Starter” product described here:
<https://www.indiamart.com/mobitech-wireless/agriculture-automations.html>
6. How much faster would an octa-core smart-phone be compared to a dual-core smart-phone?
7. Consider the following definition of a C structure.

```
struct props {
    int x; // size 32 bits
    long int a; // size 64 bits
    char *y; // size 32 bits
};
```

Give this structure definition, translate the following C code into MIPS assembly code.

```
int len = 100;
struct props M[100];
int i;
struct props *ptr;
for(i = 0; i < len; i++) {
    ptr = &M[i];
    ptr->x = 65539;
    ptr->a = 281487861612544L; // 65539 * 65536 * 65536
    ptr->y = i+3;
} // End for()
```

8. [Based on Q2.14 from the text] Translate the following C code segment to MIPS assembly language:

```
while (save[i] == k) { i = i + 1; }
```

- (a) First, using a conditional branch at the top of the loop and one unconditional branch at the bottom of the loop.
 - (b) Next, an equivalent code using only one conditional branch per loop execution.
 - (c) What is the static code size in each case?
 - (d) How many instructions are executed in each case, if the number of iterations of the loop is 10 (i.e., $\text{save}[i + 10 * j]$ does not equal k but $\text{save}[i], \dots, \text{save}[i + 9 * j]$ equal k)?
9. What does the acronym MIPS (the processor) stand for?
 10. In which classes of computing platforms is MIPS popular today?

CS305: Computer Architecture

Tutorial 03, [Thu 27 Jul, Mon 31 Jul, Tue 01 Aug]

Concepts tested: Instruction Encoding, Function Call Support, HLL Code to Process

1. An assembly program has three functions as outlined below.

main:	F:	G:
...
# read \$a0, \$a1	# read \$a0, \$a1	# set \$s3
...	# set \$s0, \$s1	...
# set \$s0, \$a0, \$a1	# set \$t0, \$t1	# set \$t1
# set \$s1, \$t0	...	# set \$ra (unusual)
...	jal G	...
jal F	...	# read \$s3, \$t1
# read \$v0, \$s0, \$a0	# read \$t1	...
...	# read \$s0, \$s1, \$a0	jr \$ra
jr \$ra	...	
	jr \$ra	

- (a) Which registers does main have to save as caller? As callee?
 - (b) Which registers does F have to save as caller? As callee?
 - (c) Which registers does G have to save as caller? As callee?
2. If the number of registers in MIPS is increased to 64, what implication does it have on the instruction encoding?
 3. What is the maximum array index which can be supported as a constant in a single load instruction? Assume that the array is of 32-bit integers.
 4. Suppose that program P is written in 2 files $p1.s$ & $p2.s$. It has no other external library. And program Q is written in 2 files $q1.s$ and $q2.s$. Q has to be linked with an external library $lib1.o$ before being executed. Answer the following questions.
 - (a) While generating the object files $p1.o$ & $p2.o$ for P , can the assembler exchange every instance of $\$s0$ with $\$s1$ (i.e. use $\$s1$ wherever $\$s0$ appears, and vice versa)? What about while generating the object files $q1.o$ & $q2.o$? You can assume (for both P and Q) that no unresolved instruction (i.e. in the relocation table) uses the two registers in question. Explain your answer briefly.
 - (b) Answer the above question for the case when the two registers being exchanged are $\$s0$ and $\$t0$. Explain your answer briefly.

CS230: Digital Logic Design and Computer Architecture

Tutorial 03 [Mon 02 Sep, Tue 03 Sep, Thu 05 Sep]

Concepts tested: Computer Arithmetic in MIPS, Computer Performance Quantification, Single Cycle Implementation

1. Consider the following Java code fragment:

```
for(i = k; i < N; i++) { a[i] = b[i] + c; }
```

Assume that 'a' and 'b' are arrays of words. Also assume that the base address of 'a' and 'b' are in \$a0 and \$a1 respectively. Register \$t0 is associated with 'i', \$t1 with 'k', \$t2 with 'N', and register \$s0 with the value of 'c'. Assume that the (maximum allocated) lengths of arrays 'a' and 'b' are in \$a2 and \$a3 respectively.

- (a) Translate the above code into MIPS assembly code. Comment your code appropriately, and use intuitive label names. You have to check for memory out-of-bounds exception before each array reference. If there is any out-of-bounds exception, you should break out of the loop by jumping to a label called 'OutOfBounds'. Write the code without any optimization taking advantage of MIPS's 2's complement representation.
- (b) What optimization can you make in the above code to take advantage of 2's complement representation, while doing the out-of-bounds check?
- (c) Suppose you want to further optimize the above code by extending the MIPS ISA. To the ISA, we want to add instructions `lw_inc` and `sw_inc`, which increment something in addition to loading/storing. What is this something which must be incremented by the instruction? And what should be the default increment value?
- (d) Which of `sw_inc` and/or `lw_inc` can you use in the above code to optimize it? How?

2. MIPS code performance analysis

For this question, take the code segment from the previous question. And assume that the 2's complement-based optimization in part (b) of the above question always applies.

- (a) How many instructions does the optimized code from (b) execute, assuming that there are no out-of-bounds exception? Give your answer in terms of appropriate symbols, as necessary.
- (b) What is the new instruction execution count after using `sw_inc` and/or `lw_inc` in (d)?
- (c) Suppose that the addition of `sw_inc/lw_inc` to the ISA results in an factor of 'x' increase in the clock period. For what values of 'x' does the use of `sw_inc/lw_inc` improve the performance of the above code segment? For what values of 'x' does it degrade the performance?

3. **[Based on Q4.11 from the text]** Consider program P which runs on a 1 Ghz machine M in 10 sec. An optimization is made to P, replacing all instances of multiplying a value by 4 (`mult X, X, 4`) with two instructions that set X to X+X twice (`add X, X, X; add X, X, X`). Call this optimized program P1. The CPI of a multiply instruction is 4, and the CPI of an add is 1. After recompiling, the program now runs in 9 sec on M.

- (a) How many executed multiplies were replaced by the compiler?
- (b) What is the minimum possible increase in static code size when going from P to P1?

4. The following is a C++ implementation of a method for computing the square root of a given number (assumed positive).

```
float sqrt(float x) {  
    float est = 1;  
    while ((est*est) != x) { est = 0.5*(est + x/est); }  
    return est;  
}
```

- (a) What is wrong with the above code and how can you correct it?
- (b) What is the name (in Mathematics) of the algorithm logically implemented by the given algorithm? (Up to 3HP for the first three who identify the name and tell the instructor during the tutorial).

5. Draw the hardware diagram for the single cycle implementation of the MIPS instruction subset `add`, `sub`, `and`, `or`, `slt`, `lw`, `sw`, `beq`.

CS230: Digital Logic Design and Computer Architecture

Tutorial 04 [Mon 09 Sep, Tue 10 Sep]

Concepts tested: Single Cycle Implementation, Extension

1. Draw the hardware diagram for the single cycle implementation of the MIPS instruction subset **add**, **sub**, **and**, **or**, **slt**, **lw**, **sw**, **beq**.
2. Identify the control lines in the above implementation and draw the truth table for the (main) control unit.
3. Extend the above datapath to support **{lb, lbu}**; that is, the signed and unsigned versions of the load-byte instruction. Show *only the changes* to the original datapath.
4. Show the modified truth table to generate the controls; mention just the changes/additions from the earlier table.
5. Extend the original datapath to support a new instruction **ldpc**, which loads the value of **PC+4** onto a given register (no need to include support for **lb**, **lbu** here).
6. Show the modified truth table to generate the controls; mention just the changes/additions from the earlier table.