




CS230: Digital Logic Design and Computer Architecture

Lecture 5: The D-Day@Digital logic

<https://www.cse.iitb.ac.in/~biswa/courses/CS230/autumn23/main.html>




<https://www.cse.iitb.ac.in/~biswa/>

 Phones
(smart/non-smart)
on silence plz,
Thanks



Recap of D Flip-flop

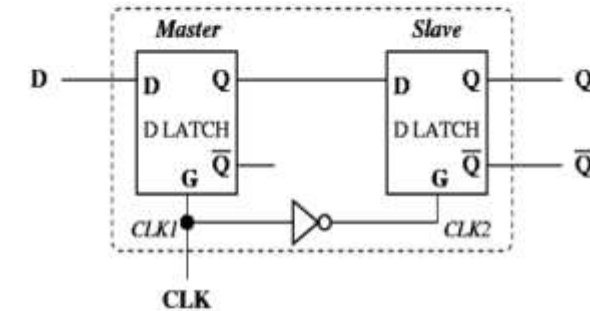  - **Example:** When CLK is high, output of master is allowed to change with D; when CLK is low (falling edge), the output of the master is fixed and propagated through to the output of the slave \Rightarrow this flip-flop triggers on *falling or negative edge*.





CLK	D	Q^*	\overline{Q}^*
\downarrow	0	0	1
\downarrow	1	1	0

Characteristic Table

Recap of D Flip-flop

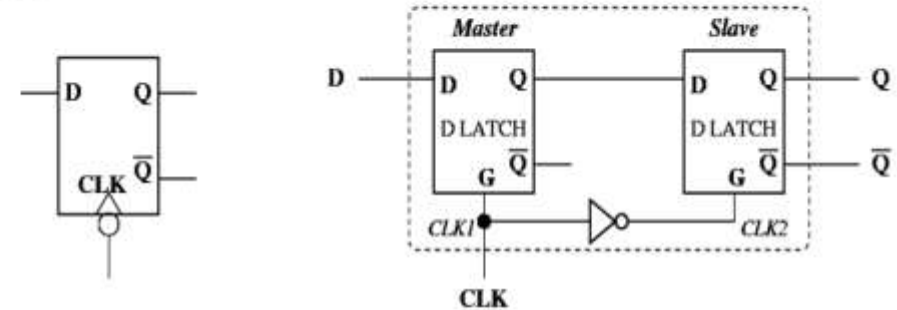 - **Example:** When CLK is high, output of master is allowed to change with D; when CLK is low (falling edge), the output of the master is fixed and propagated through to the output of the slave \Rightarrow this flip-flop triggers on *falling or negative edge*.





CLK	D	Q*	\overline{Q}^*
\downarrow	0	0	1
\downarrow	1	1	0

Characteristic Table

Recap of D Flip-flop

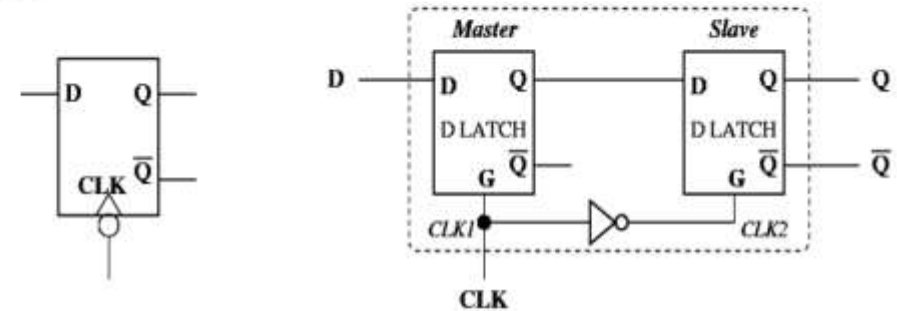 - **Example:** When CLK is high, output of master is allowed to change with D; when CLK is low (falling edge), the output of the master is fixed and propagated through to the output of the slave \Rightarrow this flip-flop triggers on *falling or negative edge*.





CLK	D	Q*	\bar{Q}^*
↓	0	0	1
↓	1	1	0

Characteristic Table

Recap of D Flip-flop

  - **Example:** When CLK is high, output of master is allowed to change with D; when CLK is low (falling edge), the output of the master is fixed and propagated through to the output of the slave \Rightarrow this flip-flop triggers on *falling or negative edge*.





CLK	D	Q*	\overline{Q}^*
\downarrow	0	0	1
\downarrow	1	1	0

Characteristic Table

Recap of D Flip-flop

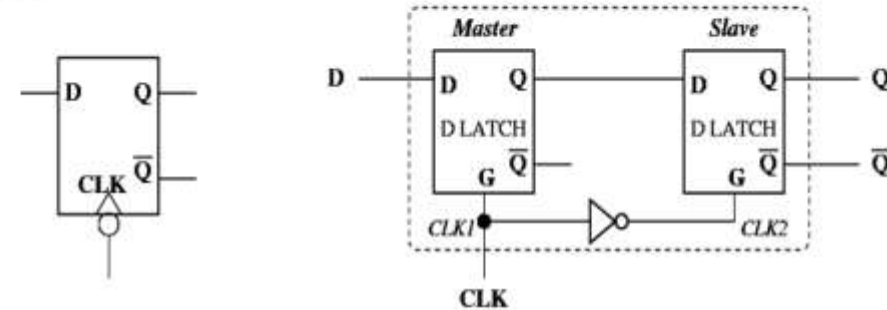 - **Example:** When CLK is high, output of master is allowed to change with D; when CLK is low (falling edge), the output of the master is fixed and propagated through to the output of the slave \Rightarrow this flip-flop triggers on *falling or negative edge*.



CLK	D	Q*	\bar{Q}^*
\downarrow	0	0	1
\downarrow	1	1	0

Characteristic Table

Delay to make sure all is well


- **Setup time, t_{su}** , is the time period prior to the clock becoming active (edge or level) during which the flip-flop inputs must remain stable.
- **Hold time, t_h** , is the time after the clock becomes inactive during which the flip-flop inputs must remain stable.
- Setup time and hold time define a *window of time during which the flip-flop inputs cannot change* – quiescent interval.

More Delay

- **Propagation delay**, t_{pHL} and t_{pLH} , has the same meaning as in combinational circuit – beware propagation delays usually will not be equal for all input to output pairs. There can be two propagation delays: t_{C-Q} (*clock*→Q delay) and t_{D-Q} (*data*→Q delay).
- For a level or pulse triggered latch:
 - Data input should remain stable till the clock becomes inactive.
 - Clock should remain active till the input change is propagated to Q output. That is, active period of the clock,


$$t_w > \max \{t_{pLH}, t_{pHL}\}$$


All in One

 

D Flip-flop (edge-triggered)
(positive edge triggering)

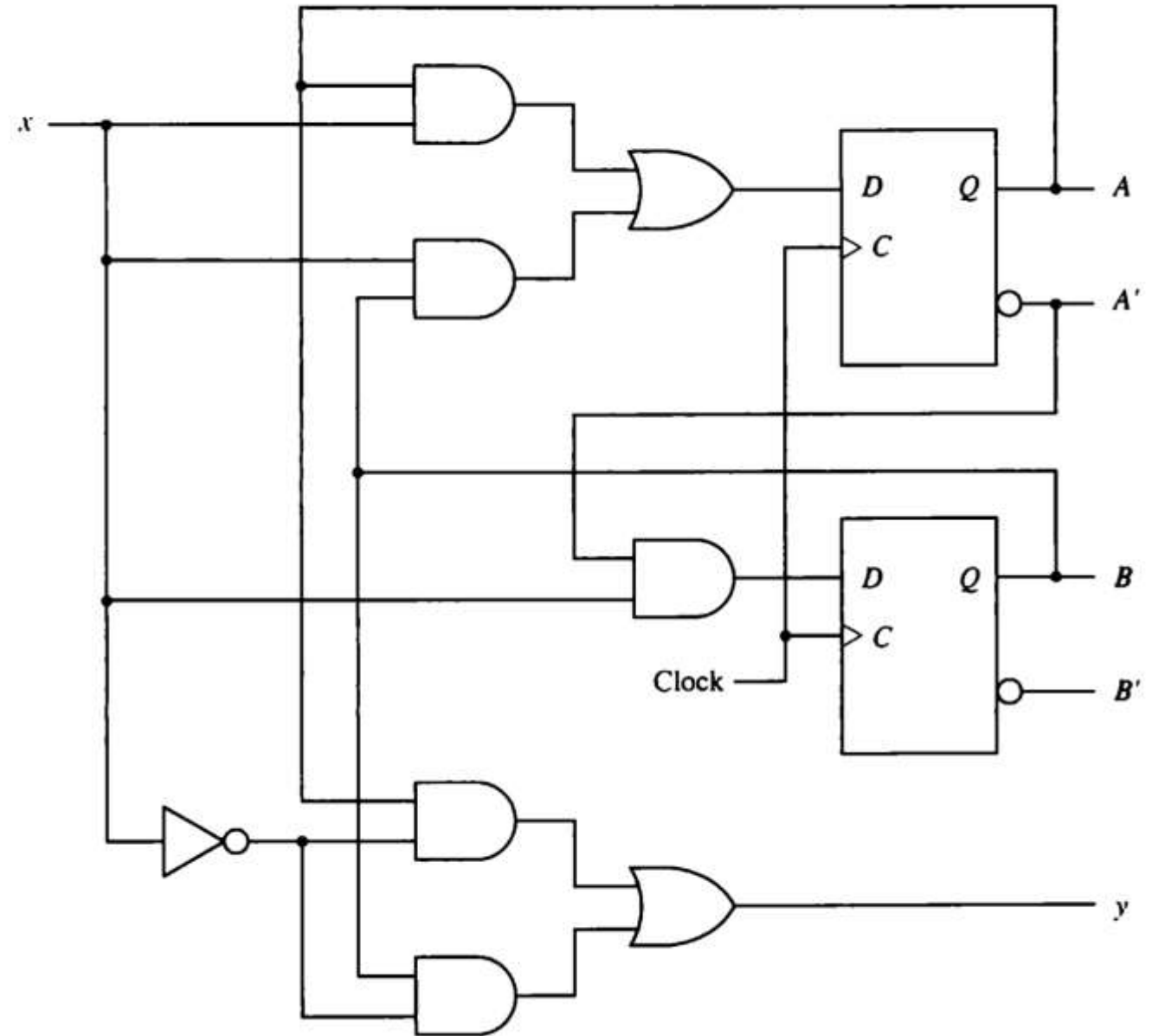Revisiting sequential circuit: A complete picture



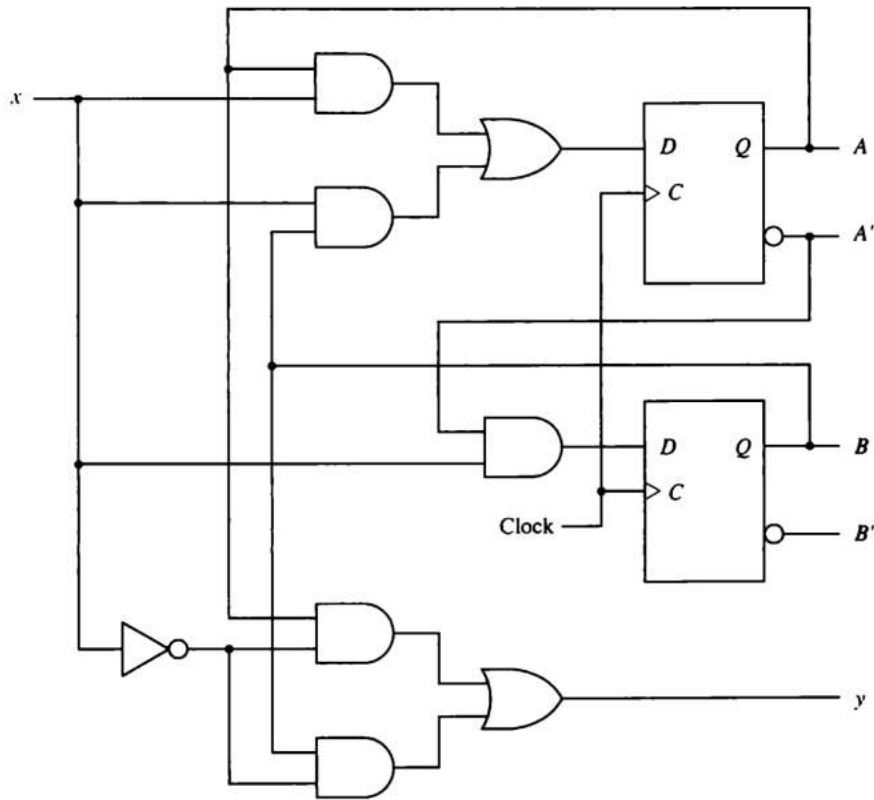


Present state		Input x	Next state		Output y
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0


$$A(t+1) = Ax + Bx, B(t+1) = A'x, y = Ax' + Bx'$$

State Table

State Diagram

 
x/y where x is
input and y is
output after
the transition





Try it for a
binary
counter 😊

Lab-1



World of State machines (FSMs) Moore and Mealy Machines

Moore vs Mealy




Moore machine: Output depends on the current state



Mealy machine: Output depends on the current state and inputs


Odd Parity Checker

Moore

 

- Serial input string
 - OUT=1 if odd # of 1s in input
 - OUT=0 if even # of 1s in input
- Let's do this for Moore and Mealy

Mealy

 



Try on your own

State Transitions

Output changes only when the state changes
Appears after the state transition takes place
outputs change at clock edge

Even = 0

Odd = 1

Moore


Present State	Input	Next State	Present State
Even	0	Even	0
Even	1	Odd	0
Odd	0	Odd	1
Odd	1	Even	1

Output changes when the state and input changes
Appears before the state transition is completed
React faster to inputs — don't wait for clock

Mealy


Present State	Input	Next State	Present State
Even	0	Even	0
Even	1	Odd	1
Odd	0	Odd	1
Odd	1	Even	0

01/10 detector: Moore Machine

 

reset	input	current state	next state	current output
1	—	—	A	0
0	0	A	B	0
0	1	A	C	0
0	0	B	B	0
0	1	B	D	0
0	0	C	E	0
0	1	C	C	0
0	0	D	E	1
0	1	D	C	1
0	0	E	B	1
0	1	E	D	1

01/10 detector: Mealy Machine

 

reset	input	current state	next state	current output
1	—	—	A	0
0	0	A	B	0
0	1	A	C	0
0	0	B	B	0
0	1	B	C	1
0	0	C	B	1
0	1	C	C	0

PAUSE



Architecture-101

Next Few Lectures



HOW CAN A
PROGRAMME
R INTERACT
WITH THE
PROCESSOR?



THE
LANGUAGE
OF
COMPUTER:
INSTRUCTION
S



INSTRUCTION
S HAVE A
VOCABULARY
CALLED
INSTRUCTION
SET



DRIVEN BY
INSTRUCTION
SET
ARCHITECTUR
E (ISA)



ISA: X86,
ARM, RISC-V,
MIPS

Coffee Credits

- Anirrudh + 1
- Tejas +1

