

CS305

Computer Architecture

Control Logic for the Multi-Cycle MIPS Implementation

Bhaskaran Raman
Room 406, KR Building
Department of CSE, IIT Bombay

<http://www.cse.iitb.ac.in/~br>

Summary of Control Lines

Single Cycle

RegWr: 0=disable, 1=enable

RegDst: 0=Rd, 1=Rt

Mem2Reg: 0=ALUOut, 1=MemOut

ALUSrc: 0=Reg2Val, 1=SgnExtImm

ALUOp2: 00=add, 01=sub, 10=reg-reg

MemRd, MemWr: 0=disable, 1=enable

Branch: 0 for other instrns, 1 for beq

Multi-Cycle

RegWr: 0=disable, 1=enable

RegDst: 0=Rd, 1=Rt

Mem2Reg: 0=ALUOut, 1=MDR

ALUIp1Ctl: 0=Reg1Val, 1=PC

*ALUIp2Ctl2: 00=Reg2Val, 01=4,
10=SgnExtImm, 10=SgnExtImmShft2*

ALUOp2: 00=add, 01=sub, 10=reg-reg

MemRd, MemWr: 0=disable, 1=enable

IorD: 0=PC, 1=ALUOut

IRWr: 0=disable, 1=enable

MDRWr: 0=disable, 1=enable (not needed)

PCSrc: 0=OutputOfALU, 1=ALUOut

PCWr: 0=disable, 1=enable

Reg
File

ALU

Mem

PC
write

Generating Control Lines

- Generate control lines as per the execution plan
- Control lines are a function of what happens in each stage in each instruction (i.e. the execution plan)

Control Lines in Stage-1

Stage-1:

(a) Instruction fetch

IR = Mem[PC]

(b) PC = PC+4

RegWr: 0=disable, 1=enable

RegDst: 0=Rd, 1=Rt

Mem2Reg: 0=ALUOut, 1=MDR

ALUIp1Ctl: 0=Reg1Val, 1=PC

ALUIp2Ctl2: 00=Reg2Val, 01=4,
10=SgnExtImm, 10=SgnExtImmShft2

ALUOp2: 00=add, 01=sub, 10=reg-reg

MemRd: 0=disable, 1=enable

MemWr: 0=disable, 1=enable

lorD: 0=PC, 1=ALUOut

IRWr: 0=disable, 1=enable

PCSrc: 0=OutputOfALU, 1=ALUOut

PCWr: 0=disable, 1=enable

Control Lines in Stage-2

Stage-2:

(a) Register read

Reg1T = Reg[Rs]

Reg2T = Reg[Rt]

(b) Compute BrTgt

ALUOut =

(PC+4) + SgnExtImmShift2

RegWr: **0=disable**, 1=enable

RegDst: 0=Rd, 1=Rt

Mem2Reg: 0=ALUOut, 1=MDR

*ALUIp1Ctl: 0=Reg1Val, **1=PC***

*ALUIp2Ctl2: 00=Reg2Val, 01=4,
10=SgnExtImm, **10=SgnExtImmShft2***

ALUOp2: **00=add**, 01=sub, 10=reg-reg

MemRd: **0=disable**, 1=enable

MemWr: **0=disable**, 1=enable

lorD: 0=PC, 1=ALUOut

*IRWr: **0=disable**, 1=enable*

PCSrc: 0=OutputOfALU, 1=ALUOut

*PCWr: **0=disable**, 1=enable*

Control Lines in Stage-3: reg-reg

Stage-3: reg-reg

(a) ALU operation

ALUOut = Reg1T op Reg2T

RegWr: 0=disable, 1=enable

RegDst: 0=Rd, 1=Rt

Mem2Reg: 0=ALUOut, 1=MDR

ALUp1Ctl: 0=Reg1Val, 1=PC

ALUp2Ctl2: 00=Reg2Val, 01=4,
10=SgnExtImm, 10=SgnExtImmShft2

ALUOp2: 00=add, 01=sub, 10=reg-reg

MemRd: 0=disable, 1=enable

MemWr: 0=disable, 1=enable

IorD: 0=PC, 1=ALUOut

IRWr: 0=disable, 1=enable

PCSrc: 0=OutputOfALU, 1=ALUOut

PCWr: 0=disable, 1=enable

Control Lines in Stage-3: lw, sw

Stage-3: lw, sw

(a) Mem addr computation

$$\text{ALUOut} = \text{Reg1T} + \text{SgnExtImm}$$

RegWr: 0=disable, 1=enable

RegDst: 0=Rd, 1=Rt

Mem2Reg: 0=ALUOut, 1=MDR

ALUp1Ctl: 0=Reg1Val, 1=PC

ALUp2Ctl2: 00=Reg2Val, 01=4,
10=SgnExtImm, 10=SgnExtImmShft2

ALUOp2: 00=add, 01=sub, 10=reg-reg

MemRd: 0=disable, 1=enable

MemWr: 0=disable, 1=enable

IorD: 0=PC, 1=ALUOut

IRWr: 0=disable, 1=enable

PCSrc: 0=OutputOfALU, 1=ALUOut

PCWr: 0=disable, 1=enable

Control Lines in Stage-3: beq

Stage-3: beq

(a) Branch condition check

$$\text{ALUOut} = \text{Reg1T} - \text{Reg2T}$$

$$\text{zero?} = (\text{ALUOut} \neq 0)$$

(b) If zero?, PC = BrTgt (ALUOut)

RegWr: 0=disable, 1=enable

RegDst: 0=Rd, 1=Rt

Mem2Reg: 0=ALUOut, 1=MDR

ALUp1Ctl: 0=Reg1Val, 1=PC

ALUp2Ctl2: 00=Reg2Val, 01=4,
10=SgnExtImm, 10=SgnExtImmShft2

ALUOp2: 00=add, 01=sub, 10=reg-reg

MemRd: 0=disable, 1=enable

MemWr: 0=disable, 1=enable

lorD: 0=PC, 1=ALUOut

IRWr: 0=disable, 1=enable

PCSrc: 0=OutputOfALU, 1=ALUOut

PCWr: 0=disable, 1=enable zero?

Control Lines in Stage-4: reg-reg

Stage-4: reg-reg

(a) Write back ALUOut to RegFile

RegWr: 0=disable, 1=enable

RegDst: 0=Rd, 1=Rt

Mem2Reg: 0=ALUOut, 1=MDR

ALUp1Ctl: 0=Reg1Val, 1=PC

*ALUp2Ctl2: 00=Reg2Val, 01=4,
10=SgnExtImm, 10=SgnExtImmShft2*

ALUOp2: 00=add, 01=sub, 10=reg-reg

MemRd: 0=disable, 1=enable

MemWr: 0=disable, 1=enable

lorD: 0=PC, 1=ALUOut

IRWr: 0=disable, 1=enable

PCSrc: 0=OutputOfALU, 1=ALUOut

PCWr: 0=disable, 1=enable

Control Lines in Stage-4: lw

Stage-4: lw

(a) Read memory

MDR = Mem[ALUOut]

RegWr: 0=disable, 1=enable

RegDst: 0=Rd, 1=Rt

Mem2Reg: 0=ALUOut, 1=MDR

ALUp1Ctl: 0=Reg1Val, 1=PC

*ALUp2Ctl2: 00=Reg2Val, 01=4,
10=SgnExtImm, 10=SgnExtImmShft2*

ALUOp2: 00=add, 01=sub, 10=reg-reg

MemRd: 0=disable, 1=enable

MemWr: 0=disable, 1=enable

lorD: 0=PC, 1=ALUOut

IRWr: 0=disable, 1=enable

PCSrc: 0=OutputOfALU, 1=ALUOut

PCWr: 0=disable, 1=enable

Control Lines in Stage-4: sw

Stage-4: sw

(a) Write memory

Mem[ALUOut] = Reg2T

RegWr: **0=disable**, 1=enable

RegDst: 0=Rd, 1=Rt

Mem2Reg: 0=ALUOut, 1=MDR

ALUp1Ctl: 0=Reg1Val, 1=PC

*ALUp2Ctl2: 00=Reg2Val, 01=4,
10=SgnExtImm, 10=SgnExtImmShft2*

ALUOp2: 00=add, 01=sub, 10=reg-reg

MemRd: **0=disable**, 1=enable

MemWr: 0=disable, **1=enable**

lorD: 0=PC, 1=ALUOut

*IRWr: **0=disable**, 1=enable*

PCSrc: 0=OutputOfALU, 1=ALUOut

*PCWr: **0=disable**, 1=enable*

Control Lines in Stage-5: lw

Stage-5: lw

(a) Write back to RegFile from MDR

RegWr: 0=disable, 1=enable

RegDst: 0=Rd, 1=Rt

Mem2Reg: 0=ALUOut, 1=MDR

ALUp1Ctl: 0=Reg1Val, 1=PC

*ALUp2Ctl2: 00=Reg2Val, 01=4,
10=SgnExtImm, 10=SgnExtImmShft2*

ALUOp2: 00=add, 01=sub, 10=reg-reg

MemRd: 0=disable, 1=enable

MemWr: 0=disable, 1=enable


lorD: 0=PC, 1=ALUOut

IRWr: 0=disable, 1=enable


PCSrc: 0=OutputOfALU, 1=ALUOut

PCWr: 0=disable, 1=enable

Implementing the Control: State Diagram

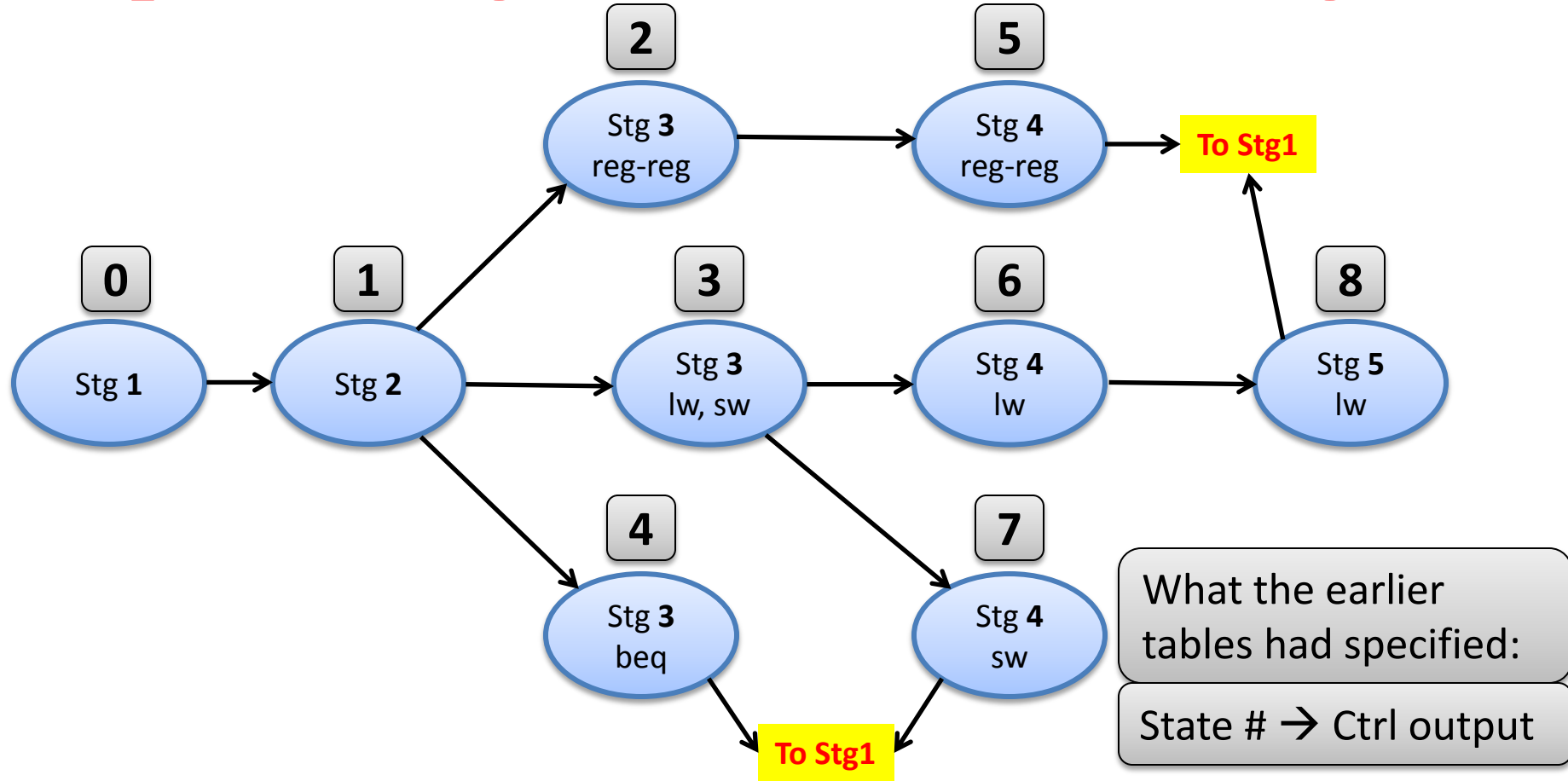

State Machine

 

We have: a Moore machine, but for beq

Moore machine, or
Mealy machine

Moore machine:
output depends on
current state

Mealy machine:
output depends on
current state & input

In both cases: next
state depends on
current state and
input

Summary

- Execution plan determines control lines
- Control logic: Moore or Mealy machine
 - More complex than single cycle case (combinational logic)