




Lecture-3: Combinational Circuits

<https://www.cse.iitb.ac.in/~biswa/courses/CS230/main.html>

<https://www.cse.iitb.ac.in/~biswa/>



Phones
(smart/non-smart)
on silence plz,
Thanks



Contd.

1. **Minterm to Maxterm conversion:**
rewrite minterm shorthand using maxterm shorthand
replace minterm indices with the indices not already used
E.g., $F(A, B, C) = \sum m(3, 4, 5, 6, 7) = \prod M(0, 1, 2)$
2. **Maxterm to Minterm conversion:**
rewrite maxterm shorthand using minterm shorthand
replace maxterm indices with the indices not already used
E.g., $F(A, B, C) = \prod M(0, 1, 2) = \sum m(3, 4, 5, 6, 7)$
3. **Expansion of F to expansion of \bar{F} :**

$$\begin{array}{ll} \text{E. g., } F(A, B, C) = \sum m(3, 4, 5, 6, 7) & \longrightarrow \bar{F}(A, B, C) = \sum m(0, 1, 2) \\ = \prod M(0, 1, 2) & \longrightarrow = \prod M(3, 4, 5, 6, 7) \end{array}$$

4. **Minterm expansion of F to Maxterm expansion of \bar{F} :**
rewrite in Maxterm form, using the same indices as F

$$\begin{array}{ll} \text{E. g., } F(A, B, C) = \sum m(3, 4, 5, 6, 7) & \longrightarrow \bar{F}(A, B, C) = \prod M(3, 4, 5, 6, 7) \\ = \prod M(0, 1, 2) & \longrightarrow = \sum m(0, 1, 2) \end{array}$$

K-Maps

- Karnaugh Map (K-map) method

- K-map is an alternative method of representing the **truth table** that helps **visualize adjacencies** in up to 6 dimensions
- Physical adjacency \leftrightarrow Logical adjacency

2-variable K-map

$A \backslash B$	0	1
0	00	01
1	10	11

3-variable K-map

$A \backslash BC$	00	01	11	10
0	000	001	011	010
1	100	101	111	110

4-variable K-map

$AB \backslash CD$	00	01	11	10
00	0000	0001	0011	0010
01	0100	0101	0111	0110
11	1100	1101	1111	1110
10	1000	1001	1011	1010

A vintage metal coffee pot with a black handle is pouring dark coffee into a clear glass cup. Steam is rising from the cup, and the scene is set on a wooden surface with a blurred background.

Coffee points

Why 11 before 10 ?




Coffee points

Why 11 before 10 ?

Numbering Scheme: 00, 01, 11, 10 is called a
“Gray Code” — only a *single bit (variable) changes*
from one code word and the next code word

How? To minimize the Function

<i>A</i> \ <i>BC</i>	00	01	11	10
	000	001	011	010
0	000	001	011	010
1	100	101	111	110

 

K-map adjacencies go “around the edges”
Wrap around from first to last column
Wrap around from top row to bottom row

How?

$CD \backslash AB$	00	01	11	10
00	1	0	0	1
01	0	1	0	0
11	1	1	1	1
10	1	1	1	1

$$F(A, B, C, D) = \sum m(0, 2, 5, 8, 9, 10, 11, 12, 13, 14, 15)$$


$$F = A + \bar{B}\bar{D} + B\bar{C}D$$

Strategy for “circling” rectangles on Kmap:

Biggest “oops!” that people forget:

Some more examples

Example: Grouping Minterms

 

Simplified Expression:

$$f(w,x,y,z) = \{m1, m3, m9, m11\} + \{m8, m12\}$$

$$= \bar{x}z + w\bar{y}z$$

Some more examples

Example: Grouping Maxterms

$f(w,x,y,z)$

		yz			
		$y+z$	$y+z'$	$y'+z'$	$y'+z$
wx		00	01	11	10
$w+x$	00	0	1	1	0
$w+x'$	01	0	0	0	0
$w'+x'$	11	1	0	0	0
$w'+x$	10	1	1	1	0

Maxterms:

- 0000 = M0
- 0010 = M2
- 0100 = M4
- 0101 = M5
- 0110 = M6
- 0111 = M7
- 1010 = M10
- 1101 = M13
- 1110 = M14
- 1111 = M15

Groupings (note: all groupings are not listed):

$\{M0, M2, M4, M6\}$, $\{M4, M5, M6, M7\}$, $\{M5, M7, M13, M15\}$,
 $\{M2, M6, M10, M14\}$, $\{M6, M7, M14, M15\}$

Simplified Expression: $f(w,x,y,z) = \{M0, M2, M4, M6\} \{M5, M7, M13, M15\}$
 $\{M2, M6, M10, M14\}$
 $= (w+z)(\bar{x}+\bar{z})(\bar{y}+z)$



Why minimize?

Efficient resource usage

Resource scarcity

Summary

- **Very simple guideline:**
 - Circle all the rectangular blocks of 1's in the map, using the fewest possible number of circles
 - Each circle should be as large as possible
 - Read off the implicants that were circled
 - Some of them may be “don't care” (X) Try it yourself

A cup of dark coffee sits on a matching saucer, placed on a light-colored surface. A wisp of steam rises from the cup. The background is composed of broad, diagonal stripes in light and dark tones. The word "PAUSE" is centered over the cup in a white, sans-serif font.

PAUSE

Combinational Circuits


- Combinational logic is often grouped into larger building blocks to build more **complex systems**
- Hides the **unnecessary gate-level details** to emphasize the function of the building block
- Output is only dependent on the input
- We now examine:
 - Decoder
 - Multiplexer
 - Full adder

Decoder

- “Input pattern detector”
- n inputs and 2^n outputs
- Exactly one of the outputs is 1 and all the rest are 0s
- The output that is logically 1 is the output corresponding to the input pattern that the logic circuit is expected to detect
- Example: 2-to-4 decoder



The complement of a decoder is encoder

A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

 


Contd.

  - n inputs and 2^n outputs
- Exactly one of the outputs is 1 and all the rest are 0s
- The output that is logically 1 is the output corresponding to the input pattern that the logic circuit is expected to detect
- Mostly decoders have an enable signal. Output is only generated if the enable is high.




- Build a 4x16 decoder using 2x4 decoders (decoder tree)..

<i>a</i>	<i>b</i>	<i>c</i>	<i>d</i>	<i>EN</i>	<i>minterm</i>
0	0	0	0	1	m0
0	0	0	1	1	m1
0	0	1	0	1	m2
0	0	1	1	1	m3
0	1	0	0	1	m4
0	1	0	1	1	m5
0	1	1	0	1	m6
0	1	1	1	1	m7
1	0	0	0	1	m8
1	0	0	1	1	m9
1	0	1	0	1	m10
1	0	1	1	1	m11
1	1	0	0	1	m12
1	1	0	1	1	m13
1	1	1	0	1	m14
1	1	1	1	1	m15
X	X	X	X	0	0

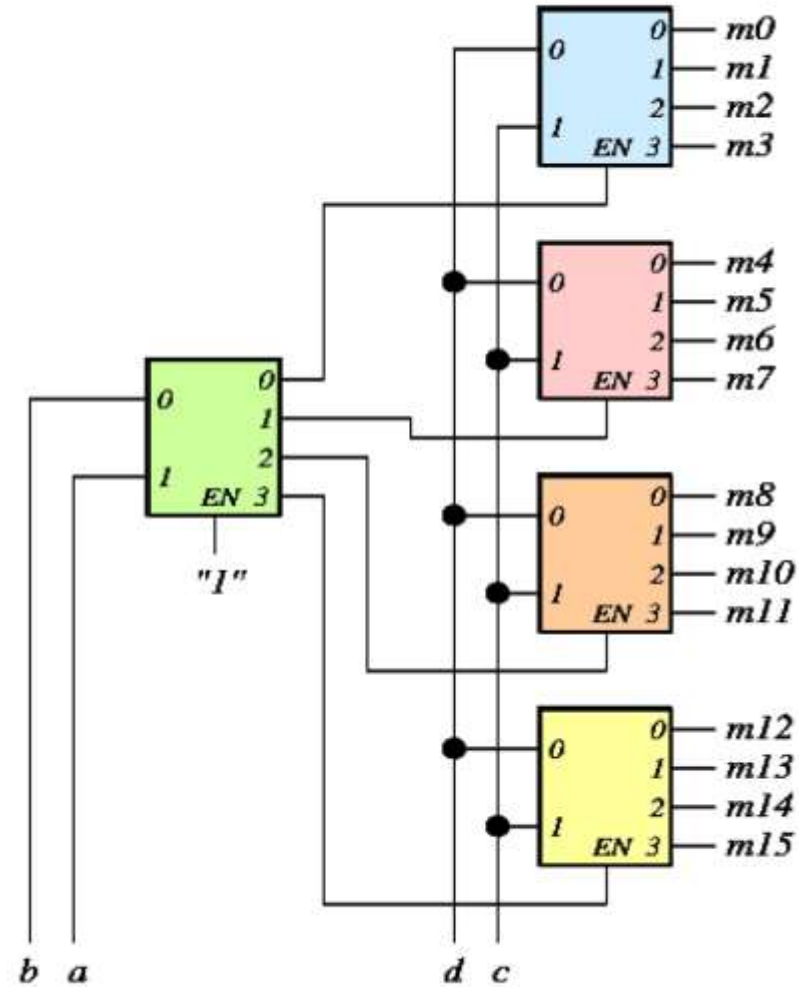

Multiplexer


 
- Selects one of the N inputs to connect it to the output
 - based on the value of a $\log_2 N$ -bit control input called select
- Example: 2-to-1 MUX
- When S is 0, Y is D_0 and when S is 1, Y is D_1





S	D_1	D_0	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Contd.

  - Selects one of the N inputs to connect it to the output
 - based on the value of a $\log_2 N$ -bit control input called select
- Example: 2-to-1 MUX




From 2 to 4:1 MUX

  

Adder


- The most basic arithmetic operation in a digital computer is addition.
- Half Adder is a combination circuit that performs addition of 2 bits.

Inputs		Outputs	
<i>a</i>	<i>b</i>	<i>Carry</i>	<i>Sum</i>
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 

$$\begin{aligned} \text{Sum} &= \bar{a}b + a\bar{b} = a \oplus b \\ \text{Carry} &= ab \end{aligned}$$

Half adder

 

$$\text{Sum} = \bar{a}b + a\bar{b} = a \oplus b$$
$$\text{Carry} = ab$$

- Half adders cannot accept a carry input and hence it is not possible to cascade them to construct an n -bit binary adder.

Full adder

- Full Adder is a combinational circuit that forms the arithmetic sum of three input bits. It is described by the following truth table:


Inputs			Outputs	
<i>c</i>	<i>b</i>	<i>a</i>	<i>C_{out}</i>	<i>Sum</i>
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1




$$\begin{aligned} \text{Sum} &= \bar{a}\bar{b}c + \bar{a}b\bar{c} + a\bar{b}\bar{c} + abc = a \oplus b \oplus c \\ C_{out} &= ab + ac + bc = ab + c(a + b) \end{aligned}$$

Implementation

 
$$\begin{aligned} \text{Sum} &= \bar{a}\bar{b}c + \bar{a}b\bar{c} + a\bar{b}\bar{c} + abc = a \oplus b \oplus c \\ C_{out} &= ab + ac + bc = ab + c(a + b) \end{aligned}$$





Full Adder at bit i

 


Ripple Carry Adder

 

Comparator (Equality Checker)

  

ALU (Arithmetic Logic Unit)

 

ALU symbol

ALU operations

$F_{2:0}$	Function
000	A AND B
001	A OR B
010	A + B
011	not used
100	A AND \bar{B}
101	A OR \bar{B}
110	A - B
111	SLT