

# CS305

## Computer Architecture


### Extending the Single Cycle MIPS Implementation

reg-reg  
lw, sw  
beq

Bhaskaran Raman  
Room 406, KR Building  
Department of CSE, IIT Bombay

<http://www.cse.iitb.ac.in/~br>

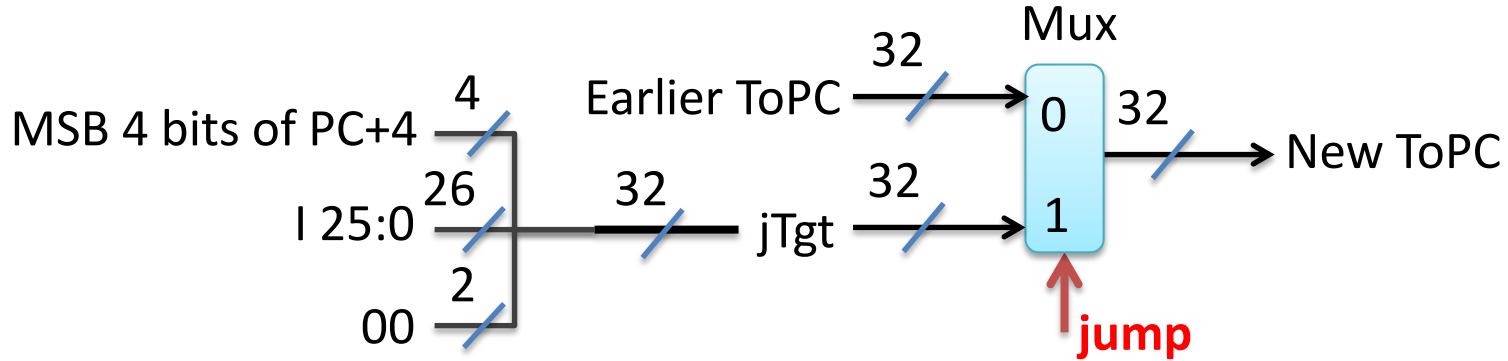
# Data Path, Control Path Extensions to Support j



# Main Control Unit Truth Table Enhancement


	RegDst	RegWr	ALUSrc	Mem-Rd	Mem-Wr	Mem2-Reg	Bran-ch	ALU-Op2	Jump
Reg-Reg	Rd (0)	1	Reg2Val (0)	0	0	ALUOut (0)	0	10	0
lw	Rt (1)	1	SgnExt-Imm (1)	1	0	MemOut (1)	0	00	0
sw	x	0	SgnExt-Imm (1)	0	1	x	0	00	0
beq	x	0	Reg2Val (0)	0	0	x	1	01	0
j	x	0	x	0	0	x	x	x	1
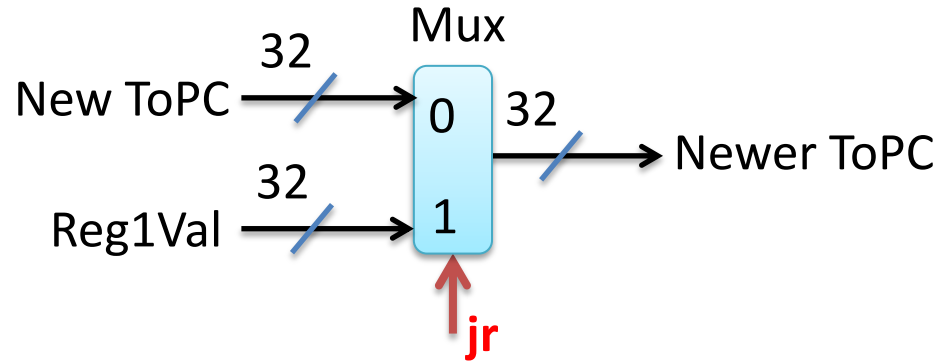
# Further Data Path, Control Path Extensions to Support jr



Main Control Unit Truth Table Enhancement										
	Reg-Dst	Reg-Wr	ALUSrc	Mem-Rd	Mem-Wr	Mem2-Reg	Bran-ch	ALU-Op2	Jump	Jr
Reg-Reg	Rd (0)	1	Reg2Val (0)	0	0	ALUOut (0)	0	10	0	0
lw	Rt (1)	1	SgnExt-Imm (1)	1	0	MemOut (1)	0	00	0	0
sw	x	0	SgnExt-Imm (1)	0	1	x	0	00	0	0
beq	x	0	Reg2Val (0)	0	0	x	1	01	0	0
j	x	0	x	0	0	x	x	x	1	0
jr	x	0	x	0	0	x	x	x	x	1
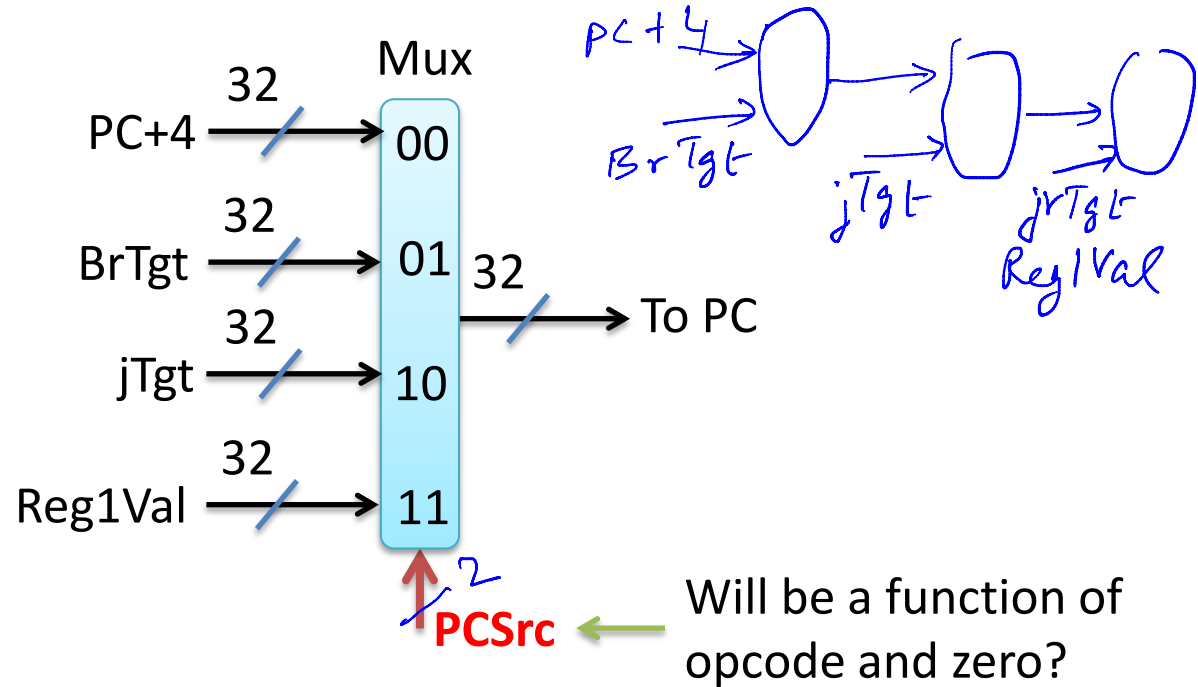
# Alternate Data Path, Control Path Modification to Support j, jr



# Summary

- The data-path and control-path can be extended to support further instructions
  - In some cases, original data-path, control-path must be modified
- Understand general principle before proceeding
  - Identify hardware component(s) for instruction
  - String them together, enhance data-path, control-path
  - Enhance/modify main control unit (truth table)